

Mathcad Solutions to Assessment Problems from Nilsson and Riedel
Electric Circuits 9th edition, © 2012 R. Doering.
 Chapter 11

AP 11.1 The voltage from A to N in a balanced three-phase circuit is $240 \angle -30^\circ$ V. If the phase sequence is positive, what is the value of V_{BC} ?

$$\angle(\text{mag}, \text{ang}) := \text{mag} \cdot (\cos(\text{ang} \cdot \text{deg}) + i \cdot \sin(\text{ang} \cdot \text{deg}))$$

$$\angle(\text{cval}) := \left(|\text{cval}| \quad \frac{\arg(\text{cval})}{\text{deg}} \right)$$

$$\sqrt{3} \cdot 240 = 415.69 \quad V_b := 240 \angle (-30 - 120) \quad V_c := 240 \angle (-30 + 120)$$

$$V_{bc} := V_b - V_c = (415.69 \quad -120) \angle$$

AP 11.2 The c-phase voltage of a balanced three-phase Y-connected system is $450 \angle -25^\circ$ V. If the phase sequence is negative, what is the value of V_{AB} ?

$$V_c := 450 \angle -25 \quad V_a := 450 \angle (-25 + 120) \quad V_b := 450 \angle (-25 - 120)$$

$$V_{ab} := V_a - V_b = (779.42 \quad 65) \angle$$

AP 11.3 The phase voltage at the terminals of a balanced three-phase Y-connected load is 2400 V.

The load has an impedance of $16 + j12 \Omega/\phi$ and is fed from a line having an impedance of $0.10 + j0.80 \Omega/\phi$. The Y-connected source at the sending end of the line has a phase sequence of acb and an internal impedance of $0.02 + j0.16 \Omega/\phi$. Use the a-phase voltage at the load as the reference and calculate (a) the line currents I_{aA} , I_{bB} , and I_{cC} ; (b) the line voltages at the source, V_{ab} , V_{bc} , and V_{ca} ; and (c) the internal phase-to-neutral voltages at the source, $V_{a'n}$, $V_{b'n}$, and $V_{c'n}$.

$$V_a := 2400 \angle 0 \quad V_c := 2400 \angle -120$$

$$V_b := 2400 \angle 120 \quad \text{Load} := (16 + j12)$$

$$\text{a) } I_{aA} := \frac{V_a}{\text{Load}} = (120 \quad -36.87) \angle$$

$$I_{bB} := \frac{V_b}{\text{Load}} = (120 \quad 83.13) \angle$$

$$I_{cC} := \frac{V_c}{\text{Load}} = (120 \quad -156.87) \angle$$

$$\text{Line} := 0.1 + j \cdot 0.8 \quad \text{Line} = (0.81 \quad 82.87) \angle$$

$$Z := 0.02 + j \cdot 0.16 \quad Z = (0.16 \quad 82.87) \angle$$

$$V_A := V_a + I_{aA} \cdot \text{Line} = (2468.18 \quad 1.62) \angle$$

$$V_B := V_b + I_{bB} \cdot \text{Line} = (2468.18 \quad 121.62) \angle$$

$$V_C := V_c + I_{cC} \cdot \text{Line} = (2468.18 \quad -118.38) \angle$$

$$\text{b) } V_{AB} := V_A - V_B = (4275.02 \quad -28.38) \angle$$

$$V_{BC} := V_B - V_C = (4275.02 \quad 91.62) \angle$$

$$V_{CA} := V_C - V_A = (4275.02 \quad -148.38) \angle$$

$$\text{c) } V_{a'n} := V_A + I_{aA} \cdot Z = (2482.05 \quad 1.93) \angle$$

$$V_{b'n} := V_B + I_{bB} \cdot Z = (2482.05 \quad 121.93) \angle$$

$$V_{c'n} := V_C + I_{cC} \cdot Z = (2482.05 \quad -118.07) \angle$$

AP 11.4 The current I_{CA} in a balanced three-phase Δ -connected load is $8 \angle -15^\circ$ A. If the phase sequence is positive, what is the value of I_{cC} ?

$$I_{CA} := 8 \angle -15 \quad I_{BC} := 8 \angle 105$$

$$8 \cdot \sqrt{3} = 13.86$$

$$I_{cC} := I_{CA} - I_{BC} = (13.86 \quad -45) \angle$$

AP 11.5 A balanced three-phase Δ -connected load is fed from a balanced three-phase circuit. The reference for the b-phase line current is toward the load. The value of the current in the b-phase is $12 \angle 65^\circ$ A. If the phase sequence is negative, what is the value of I_{AB} ?

$$I_b := 12 \angle 65 \quad I_a := 12 \angle (65 - 120) = (12 \quad -55) \angle$$

$$I_{AB} := \left(\frac{12}{\sqrt{3}} \right) \angle -85 = (6.93 \quad -85) \angle$$

$$\frac{I_a - I_b}{3} = (6.93 \quad -85) \angle$$

AP 11.6 The line voltage V_{AB} at the terminals of a balanced three-phase Δ -connected load is $4160 \angle 0^\circ$ V. The line current I_{aA} is $69.28 \angle -10^\circ$ A.

$$V_{AB} := 4160 \angle 0$$

- a) Calculate the per-phase impedance of the load if the phase sequence is positive.
 b) Repeat (a) for a negative phase sequence.

a) $I_{aA} := 69.28 \angle -10$ $I_{bB} := 69.28 \angle -130$ $I_{AB} := \frac{I_{aA} - I_{bB}}{3} = (40 \ 20) \angle$

$$Z := \frac{V_{AB}}{I_{AB}} = (104 \ -20) \angle \Omega$$

b) $I_{bB} := 69.28 \angle 110$ $I_{AB} := \frac{I_{aA} - I_{bB}}{3} = (40 \ -40) \angle$

$$Z := \frac{V_{AB}}{I_{AB}} = (104 \ 40) \angle \Omega$$

AP 11.7 The line voltage at the terminals of a balanced Δ -connected load is 110 V. Each phase of the load consists of a $3.667 \ \Omega$ resistor in parallel with a $2.75 \ \Omega$ inductive impedance. What is the magnitude of the current in the line feeding the load?

$$\|(a, b) := \frac{a \cdot b}{a + b}$$

$$Z := (3.667 \ \Omega) \parallel (j \cdot 2.75 \ \Omega) \quad I_{ab} := \frac{110V}{Z} \quad \frac{I_{ab}}{A} = (50 \ -53.13) \angle$$

$$I_{aA} := 50 \cdot \sqrt{3} = 86.6$$

AP 11.8 The three-phase average power rating of the central processing unit (CPU) on a mainframe digital computer is 22,659 W. The three-phase line supplying the computer has a line voltage rating of 208 V (rms). The line current is 73.8 A (rms). The computer absorbs magnetizing VARs.

a) Calculate the total magnetizing reactive power absorbed by the CPU.

b) Calculate the power factor.

a) $Q := \sqrt{p^2 - P^2} = 13909.5 \text{ VAR}$

b) $\frac{P}{p} = 0.85$ lagging

$$P := 22659 \text{ W}$$

$$\text{VA} \equiv \text{W}$$

$$\text{VAR} \equiv \text{W}$$

$$V_a := 208 \text{ V} \quad I_a := 73.8 \text{ A}$$

$$p := \sqrt{3} \cdot V_a \cdot I_a = 26587.67 \text{ VA}$$

AP 11.9 The complex power associated with each phase of a balanced load is $144 + j192$ kVA. The line voltage at the terminals of the load is 2450 V.

- a) What is the magnitude of the line current feeding the load?
 b) The load is delta connected, and the impedance of each phase consists of a resistance in parallel with a reactance. Calculate R and X.
 c) The load is wye connected, and the impedance of each phase consists of a resistance in series with a reactance. Calculate R and X.

$$\underline{P} := (144 + 192j) \cdot 1000$$

$$V_{an} := \frac{2450}{\sqrt{3}}$$

$$\underline{I}' := \frac{\underline{P}}{V_{an}} = 101.8 + 135.74j$$

$$\underline{I}_{aA} := \bar{\underline{I}'} = (169.67 - 53.13j) \angle$$

$$|I_{aA}| = 169.67$$

b) $\underline{R} := \frac{(2450V)^2}{144000W} = 41.68 \Omega$

$$\underline{X} := \frac{(2450V)^2}{192000 \cdot \text{VAR}} = 31.26 \Omega$$

c) $\frac{V_{an}}{I_{aA}} = 5 + 6.67j \quad \underline{R} := 5 \Omega \quad \underline{X} := 6.67 \Omega$