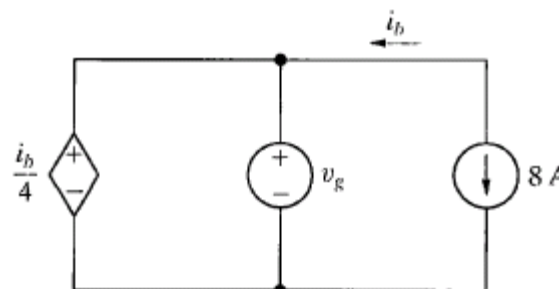


Mathcad Solutions to Assessment Problems from Nilsson and Riedel
Electric Circuits 9th edition, © 2012 R. Doering.
Chapter 2

AP 2.1 For the circuit shown,

- What value of v_g is required in order for the interconnection to be valid?
- For this value of v_g , find the power associated with the 8 A source.




a) $i_b := -8\text{A}$ $v_g := \frac{i_b}{4\text{S}} = -2\text{V}$

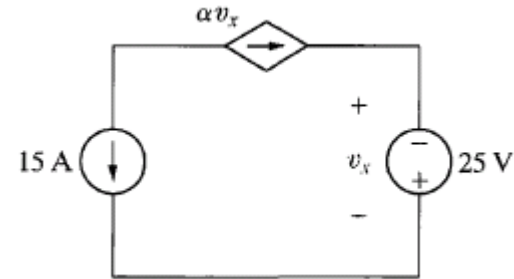b) $P := -i_b \cdot v_g = -16\text{W}$ power is delivered by the current source

AP 2.2 For the circuit shown,

- What value of α is required in order for the interconnection to be valid?
- For the value of α calculated in part (a), find the power associated with the 25 V source.




a) $v_x := -25\text{V}$

$$\alpha \cdot v_x = -15\text{A} \text{ solve, } \alpha \rightarrow \frac{3 \cdot \text{A}}{5 \cdot \text{V}} = 0.6 \text{ S}$$

b) $\underline{P} := -v_x \cdot 15\text{A} = 375 \text{ W}$ absorbed.

AP 2.3 For the circuit shown,

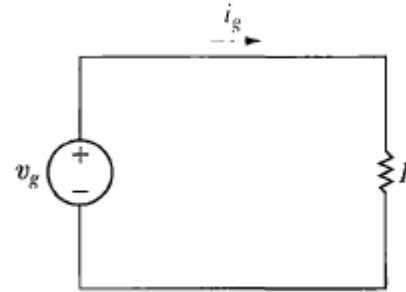
- a) If $v_g = 1 \text{ kV}$ and $i_g = 5 \text{ mA}$, find the value of R and the power absorbed by the resistor.
b) If $i_g = 75 \text{ mA}$ and the power delivered by the voltage source is 3 W , find v_g , R , and the power absorbed by the resistor.
c) If $R = 300 \Omega$ and the power absorbed by R is 480 mW , find i_g and v_g .



- a) $\underline{v_g} := 1 \text{ kV}$ $i_g := 5 \text{ mA}$ $\underline{R} := \frac{v_g}{i_g} = 200 \text{ k}\Omega$ $\underline{P} := v_g \cdot i_g = 5 \text{ W}$
- b) $\underline{i_g} := 75 \text{ mA}$ $\underline{P} := 3 \text{ W}$ $\underline{v_g} := \frac{P}{i_g} = 40 \text{ V}$ $\underline{R} := \frac{v_g}{i_g} = 533.333 \Omega$ $P = 3 \text{ W}$
- c) $\underline{R} := 300 \Omega$ $\underline{P} := 480 \text{ mW}$ $\underline{i_g} := \sqrt{\frac{P}{R}} = 40 \text{ mA}$ $\underline{v_g} := \frac{P}{i_g} = 12 \text{ V}$

AP 2.4 For the circuit shown,

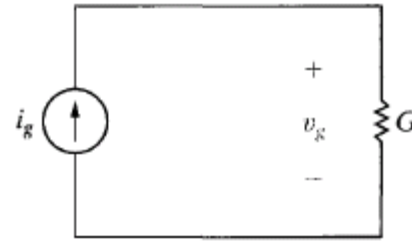- a) If $i_g = 0.5 \text{ A}$ and $G = 50 \text{ mS}$, find v_g and the power delivered by the current source.
- b) If $v_g = 15 \text{ V}$ and the power delivered to the conductor is 9 W , find the conductance G and the source current i_g .
- c) If $G = 200 \mu\text{S}$ and the power delivered to the conductance is 8 W , find i_g and v_g .




$$\text{mS} \equiv 10^{-3} \text{ S}$$
$$\mu\text{S} \equiv 10^{-6} \text{ S}$$

a) $i_g := 0.5 \text{ A}$ $G := 50 \text{ mS}$ $v_g := \frac{i_g}{G} = 10 \text{ V}$ $P := i_g \cdot v_g = 5 \text{ W}$

b) $v_g := 15 \text{ V}$ $P := 9 \text{ W}$ $G := \frac{P}{v_g^2} = 40 \text{ mS}$ $i_g := \frac{P}{v_g} = 0.6 \text{ A}$

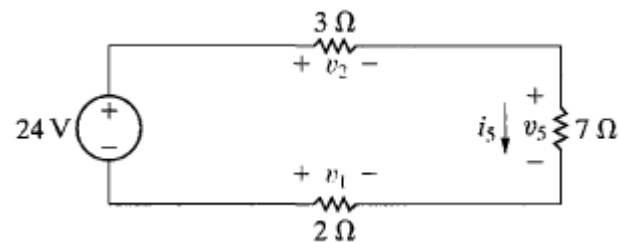c) $G := 200 \mu\text{S}$ $P := 8 \text{ W}$ $i_g := \sqrt{P \cdot G} = 40 \text{ mA}$ $v_g := \frac{P}{i_g} = 200 \text{ V}$

AP 2.5 For the circuit shown, calculate (a) i_5 ; (b) v_1 ; (c) v_2 ; (d) v_5 ; and (e) the power delivered by the 24 V source.



a) $i_5 := \frac{24\text{V}}{(3 + 7 + 2)\Omega} = 2\text{ A}$

b) $v_1 := -i_5 \cdot 2\Omega = -4\text{ V}$

c) $v_2 := i_5 \cdot 3\Omega = 6\text{ V}$

d) $v_5 := i_5 \cdot 7\Omega = 14\text{ V}$


e) $\underline{P} := 24\text{V} \cdot i_5 = 48\text{ W}$

AP 2.6 Use Ohm's law and Kirchhoff's laws to find the value of R in the circuit shown.

$$v_R := 200\text{V} - 120\text{V} = 80\text{V}$$

$$i := \frac{120\text{V}}{24\Omega} + \frac{120\text{V}}{8\Omega} = 20\text{A}$$

$$R := \frac{v_R}{i} = 4\Omega$$

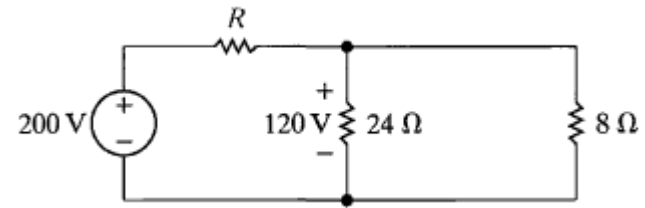


AP 2.7 a) The terminal voltage and terminal current were measured on the device shown. The values of v_t and i_t are provided in the table. Using these values, create the straight line plot of v_t versus i_t . Compute the equation of the line and use the equation to construct a circuit model for the device using an ideal voltage source and a resistor.

$$v_t := \begin{pmatrix} 25 \\ 15 \\ 5 \\ 0 \end{pmatrix} \text{V} \quad i_t := \begin{pmatrix} 0 \\ .1 \\ .2 \\ .25 \end{pmatrix} \text{A}$$

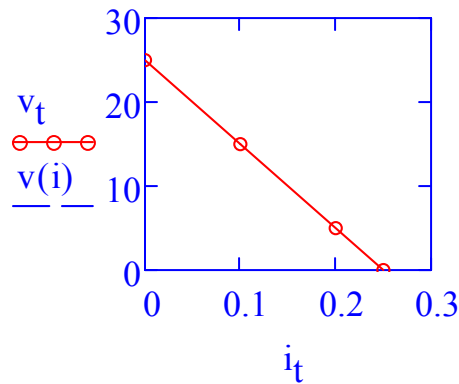
b) Use the model constructed in (a) to predict the power that the device will deliver to a 25Ω resistor.

$$v(i_t) := \frac{-25\text{V}}{.25\text{A}} \cdot i_t + 25\text{V}$$

$$\vec{v}(i_t) = \begin{pmatrix} 25 \\ 15 \\ 5 \\ 0 \end{pmatrix} \text{V}$$



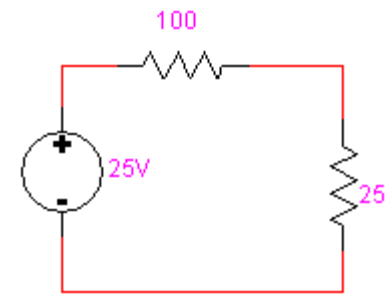a) $V_{th} := 25\text{V}$ $I_{sc} := 0.25\text{A}$ $R := \frac{V_{th}}{I_{sc}} = 100 \Omega$



b) $R_L := 25\Omega$ $V_L := \frac{25}{100 + 25} \cdot V_{th} = 5\text{V}$ $P := \frac{V_L^2}{R_L} = 1\text{W}$

AP 2.8 Repeat Assessment Problem 2.7 but use the equation of the graphed line to construct a circuit model containing an ideal current source and a resistor.

