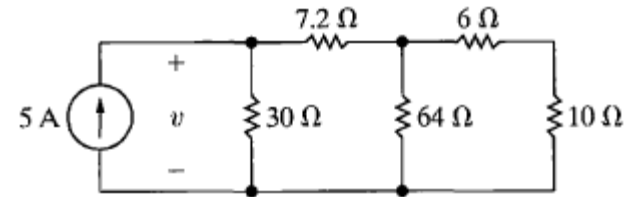


Mathcad Solutions to Assessment Problems from
 Nilsson and Riedel, *Electric Circuits* 9th edition,
 © 2012 R. Doering.
 Chapter 3

$$\|(a, b) := \frac{a \cdot b}{a + b}$$

AP 3.1 For the circuit shown, find

- the voltage v ,
- the power delivered to the circuit by the current source, and
- the power dissipated in the 10Ω resistor.



$$R := [(10 + 6) \parallel 64 + 7.2] \parallel 30 \cdot \Omega = 12 \Omega$$

$$a) \quad v := 5A \cdot R = 60 \text{ V}$$


$$b) \quad P := v \cdot 5A = 300 \text{ W}$$

$$c) \quad i_{30} := \frac{v}{30\Omega} = 2 \text{ A} \quad i_{72} := 3 \text{ A} \quad v_{72} := i_{72} \cdot 7.2\Omega = 21.6 \text{ V}$$

$$v_{64} := v - v_{72} = 38.4 \text{ V} \quad i_{64} := \frac{v_{64}}{64\Omega} = 0.6 \text{ A} \quad i_6 := i_{72} - i_{64} = 2.4 \text{ A}$$

$$i_{10} := i_6 \quad P_{10} := i_{10}^2 \cdot 10\Omega = 57.6 \text{ W}$$

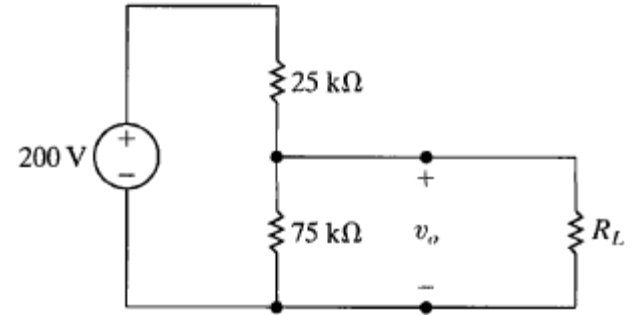- AP 3.2 a) Find the no-load value of v_o in the circuit shown.
- b) Find v_o when R_L is $150\text{ k}\Omega$.
- c) How much power is dissipated in the $25\text{ k}\Omega$ resistor if the load terminals are accidentally short-circuited?
- d) What is the maximum power dissipated in the $75\text{ k}\Omega$ resistor?




- a) $v_o := \frac{75}{75 + 25} \cdot 200\text{V} = 150\text{ V}$
- b) $v_{\text{oshort}} := \frac{(75\text{k}\Omega) \parallel (150\text{k}\Omega)}{(75\text{k}\Omega) \parallel (150\text{k}\Omega) + 25\text{k}\Omega} \cdot 200\text{V} = 133.33\text{ V}$
- c) $p := \frac{(200\text{V})^2}{25\text{k}\Omega} = 1.6\text{ W}$
- d) $p := \frac{v_o^2}{75\text{k}\Omega} = 0.3\text{ W}$

AP 3.3 a) Find the value of R that will cause 4 A of current to flow through the 80 Ω resistor in the circuit shown.

b) How much power will the resistor R from part (a) need to dissipate?

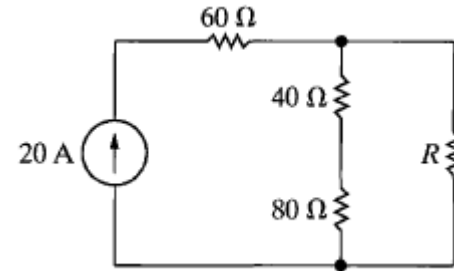c) How much power will the current source generate for the value of R from part (a)?



a) if 4A is flowing through the 40+80Ω resistors then

$$v := 4A \cdot 120\Omega = 480 \text{ V}$$

so the balance of the 20A source current must flow through R.


$$R := \frac{v}{20A - 4A} = 30 \Omega$$

b) $P := 16A \cdot v = 7.68 \text{ kW}$

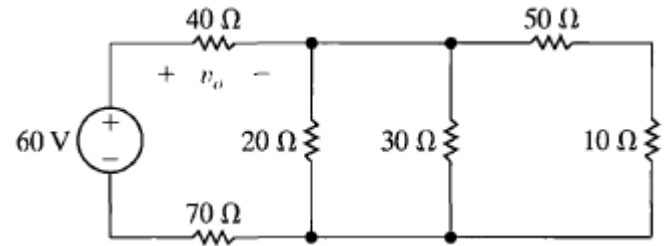c) $P := (20A \cdot 60\Omega + v) \cdot 20A = 33.6 \text{ kW}$

$$(20A)^2 (30 \parallel 120 + 60)\Omega = 33.6 \text{ kW}$$

- AP 3.4 a) Use voltage division to determine the voltage v_o across the $40\ \Omega$ resistor in the circuit shown.
- b) Use v_o from part (a) to determine the current through the $40\ \Omega$ resistor, and use this current and current division to calculate the current in the $30\ \Omega$ resistor.
- c) How much power is absorbed by the $50\ \Omega$ resistor?



$$a) \quad [(50 + 10) \parallel 30 \parallel 20] \Omega = 10 \Omega$$



$$v_o := \frac{40}{40 + 10 + 70} \cdot 60 \text{ V} = 20 \text{ V}$$

$$b) \quad i := \frac{v_o}{40 \Omega} = 0.5 \text{ A}$$

$$i_{30} := i \cdot \frac{[(50 + 10) \parallel 20]}{[(50 + 10) \parallel 20] + 30} = 166.67 \text{ mA}$$

$$c) \quad \frac{\left(i_{30} \cdot 30 \Omega \cdot \frac{50}{50 + 10} \right)^2}{50 \Omega} = 347.22 \text{ mW}$$

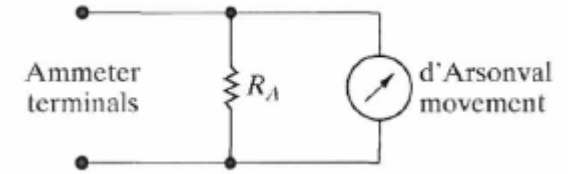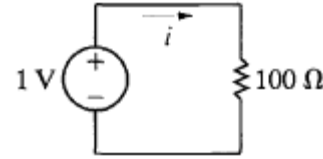- AP 3.5 a) Find the current in the circuit shown.
 b) If the ammeter in Example 3.5(a) is used to measure the current, what will it read?



a)
$$i_m := \frac{1\text{V}}{100\Omega} = 10\text{mA}$$

From example 3.5(a)
$$R_A := \frac{50}{9}\Omega$$

the movement is
$$R_m := \frac{50\text{mV}}{1\text{mA}} = 50\Omega$$



$$R_{\text{meter}} := \left[\left(\frac{50}{9} \right) \parallel 50 \right] \Omega = 5\Omega$$

so the current that will flow with the meter in series with the load resistor will be

$$i_m := \frac{1\text{V}}{105\Omega} = 9.524\text{mA}$$

AP 3.6 a) Find the voltage v across the $75\text{ k}\Omega$ resistor in the circuit shown.

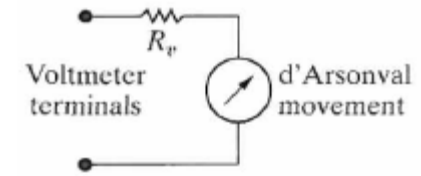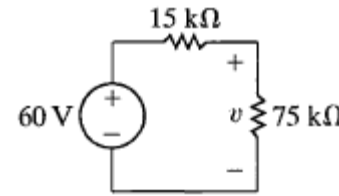b) If the 150 V voltmeter of Example 3.6(a) is used to measure the voltage, what will be the reading?



$$a) \quad v := \frac{75}{75 + 15} \cdot 60\text{V} = 50\text{V}$$

$$R_V := 1\Omega$$

$$\text{given} \quad 50\text{mV} = \frac{50\Omega}{50\Omega + R_V} \cdot 150\text{V} \quad \text{find}(R_V) = 149950\Omega$$

$$R_V := 149950\Omega \quad R_V + 50\Omega = 150\text{k}\Omega$$

$$b) \quad v_{\text{reading}} := 60\text{V} \cdot \frac{[(75\text{k}\Omega) \parallel (150\text{k}\Omega)]}{[(75\text{k}\Omega) \parallel (150\text{k}\Omega)] + 15\text{k}\Omega} = 46.15\text{V}$$


$$\frac{v_{\text{reading}}}{v} - 1 = -7.692\% \text{ error}$$

AP 3.7 The bridge circuit shown is balanced when $R_1 = 100 \Omega$, $R_2 = 1000 \Omega$, and $R_3 = 150 \Omega$.

The bridge is energized from a 5 V dc source.

a) What is the value of R_x ?

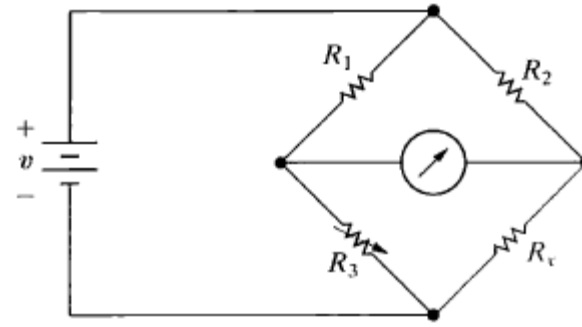b) Suppose each bridge resistor is capable of dissipating 250 mW. Can the bridge be left in the balanced state without exceeding the power-dissipating capacity of the resistors, thereby damaging the bridge?



$$R_1 := 100\Omega \quad R_2 := 1000\Omega \quad R_3 := 150\Omega$$

a)
$$\frac{R_1}{R_3} = \frac{R_2}{R_x} \quad \text{so} \quad R_x := \frac{R_2 \cdot R_3}{R_1} = 1.5 \text{ k}\Omega$$

b)
$$\frac{(5\text{V})^2}{R_1 + R_3} = 100 \text{ mW} \quad \text{so yes!}$$

AP 3.8 Use a Y-to- Δ transformation to find the voltage v in the circuit shown.

$$Y \rightarrow \Delta(R) := \begin{pmatrix} \frac{R_0 \cdot R_1 + R_1 \cdot R_2 + R_2 \cdot R_0}{R_0} \\ \frac{R_0 \cdot R_1 + R_1 \cdot R_2 + R_2 \cdot R_0}{R_1} \\ \frac{R_0 \cdot R_1 + R_1 \cdot R_2 + R_2 \cdot R_0}{R_2} \end{pmatrix}$$

$$Y \rightarrow \Delta \left[\begin{pmatrix} 20 \\ 10 \\ 5 \end{pmatrix} \Omega \right] = \begin{pmatrix} 17.5 \\ 35 \\ 70 \end{pmatrix} \Omega$$

$$\underline{R} := [(28 \parallel 70 + 17.5 \parallel 105) \parallel 35] \Omega = 17.5 \Omega$$

$$\underline{v} := 2A \cdot R = 35V$$

