

AP 6.1 The current source in the circuit shown generates the current pulse (for $t > 0$)




$$i_g(t) := \begin{cases} -300 \frac{t}{s} & 0 < t < 8 \\ 8e^{-8t} & t \geq 8 \end{cases} \text{ A}$$

Find (a) $v(0)$; (b) the instant of time, greater than zero, when the voltage v passes through zero; (c) the expression for the power delivered to the inductor; (d) the instant when the power delivered to the inductor is maximum; (e) the maximum power; (f) the instant of time when the stored energy is maximum; and (g) the maximum energy stored in the inductor.

a)

$$v(t) := 4\text{mH} \cdot \frac{d}{dt} i(t) \rightarrow -4 \cdot \text{A} \cdot \text{mH} \cdot \left(\frac{-300 \cdot t}{s} - \frac{9600 \cdot e^{-8t}}{s} \right)$$

$$v(0) = 28.8 \text{ V}$$

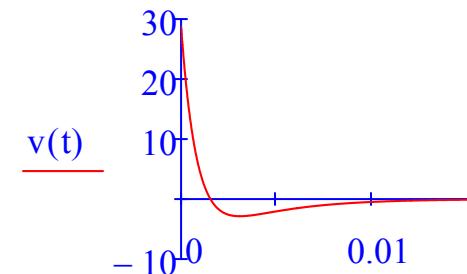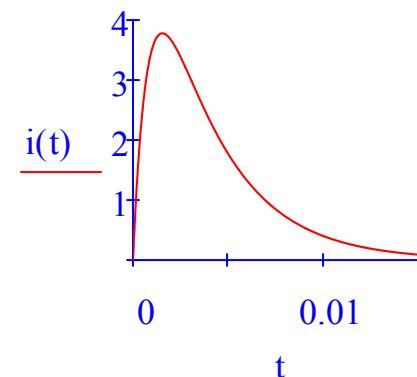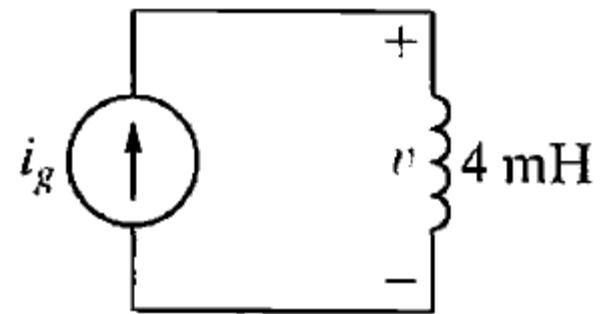


b) Given $t_{zv} := 1\text{ms}$ $v(t_{zv}) = 0$ $t_{zv} := \text{Find}(t_{zv}) = 1.54\cdot\text{ms}$

$$c) \quad p(t) := v(t) \cdot i(t) \text{ expand} \rightarrow \frac{384000 \cdot A^2 \cdot mH \cdot e^{-\frac{1500 \cdot t}{s}}}{s} - \frac{76800 \cdot A^2 \cdot mH \cdot e^{-\frac{600 \cdot t}{s}}}{s} - \frac{307200 \cdot A^2 \cdot mH \cdot e^{-\frac{2400 \cdot t}{s}}}{s}$$

$$\frac{A^2 \cdot mH}{s} = 1 \cdot mW$$

$$p(t) := \left(384 \cdot e^{-\frac{1500 \cdot t}{s}} - 76.8 \cdot e^{-\frac{600 \cdot t}{s}} - 307.2 \cdot e^{-\frac{2400 \cdot t}{s}} \right) W$$

while $t > 0$

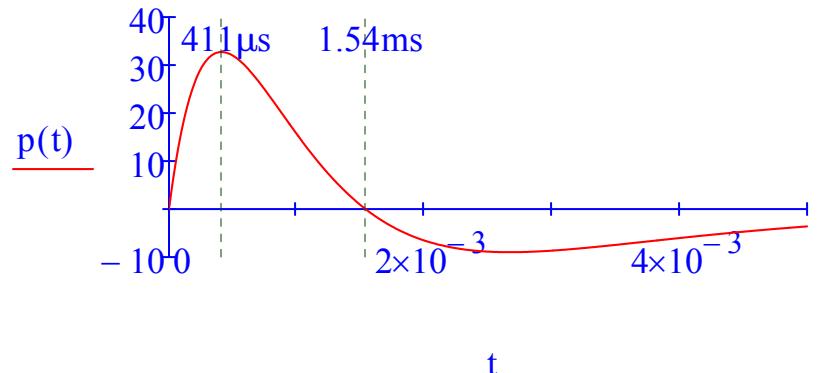

$$d) \quad \text{Given } t_{pm} := 0s \quad \frac{d}{dt}_{pm} p(t_{pm}) = 0 \quad t_{pmax} := \text{Find}(t_{pm}) = 411.051 \cdot \mu s$$

$$e) \quad p(t_{pmax}) = 32.719 \text{ W}$$

$$f) \quad \text{Given } t_{em} := 1 \text{ ms} \quad p(t_{em}) = 0 \quad t_{emax} := \text{Find}(t_{em}) = 1.54 \cdot \text{ms}$$


$$g) \quad \int_0^{t_{emax}} p(t) dt = 28.573 \cdot \text{mJ}$$

AP 6.2 The voltage at the terminals of a $0.6 \mu\text{F}$ capacitor is 0 for $t < 0$ and

$$v(t) := 40 \cdot e^{-15000 \frac{t}{s}} \cdot \sin\left(30000 \frac{t}{s}\right) \text{ V}$$

Find

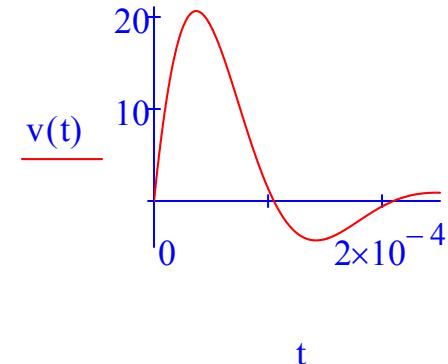- (a) $i(0)$;
- (b) the power delivered to the capacitor at $t = \pi/80 \text{ ms}$;
- (c) the energy stored in the capacitor at $t = \pi/80 \text{ ms}$.



a)



$$i(t) := 0.6 \mu\text{F} \cdot \frac{d}{dt} v(t) \rightarrow 0.6 \cdot \mu\text{F} \cdot \left(\frac{1200000 \cdot \text{V} \cdot \cos\left(\frac{30000 \cdot t}{s}\right) \cdot e^{-\frac{15000 \cdot t}{s}}}{s} - \frac{600000 \cdot \text{V} \cdot \sin\left(\frac{30000 \cdot t}{s}\right) \cdot e^{-\frac{15000 \cdot t}{s}}}{s} \right)$$

$$i(0) = 0.72 \cdot \text{A}$$

b) $p(t) := v(t) \cdot i(t)$

$$p\left(\frac{\pi}{80} \text{ ms}\right) = -649.2 \cdot \text{mW}$$

c) $\int_0^{\frac{\pi}{80} \text{ ms}} p(t) dt = 126.13 \cdot \mu\text{J}$

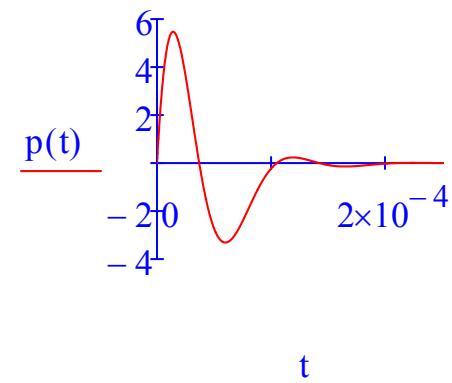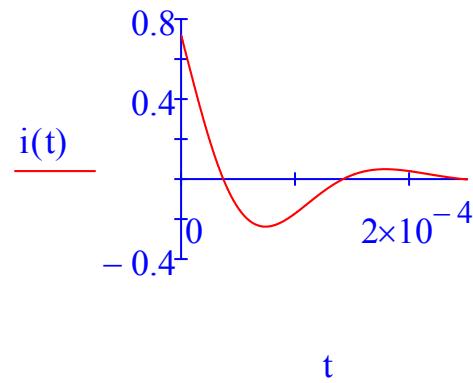

AP 6.3 The current in a $0.6\mu\text{F}$ capacitor is 0 for $t < 0$
and $3 \cos 50,000t$ A for $t > 0$.

$$C_1 := 0.6\mu\text{F}$$

$$\text{i}(t) := 3 \cos\left(50000 \frac{t}{s}\right) \text{A} \quad \text{for } t \geq 0$$

Find (a) $v(t)$

- (b) the maximum power delivered to the capacitor at any one instant of time; and
- (c) the maximum energy stored in the capacitor at any one instant of time.

a) $\int 3 \cos(500t) dt \rightarrow \frac{3 \cdot \sin(500 \cdot t)}{500}$


$$v(t) := \frac{1}{C_1} \cdot \frac{3}{50000} \cdot \sin\left(50000 \frac{t}{s}\right) \cdot \text{A} \cdot \text{s} \quad v(0) = 0 \text{ V}$$

b) $p(t) := i(t) \cdot v(t)$

$$p(t) \text{ simplify} \rightarrow \frac{0.00015 \cdot \text{A}^2 \cdot \text{s} \cdot \sin\left(\frac{100000.0 \cdot t}{s}\right)}{\mu\text{F}}$$

$$\frac{\text{A}^2 \text{s}}{\text{F}} = 1 \text{ W} \quad p(t) := 150 \sin\left(100000 \frac{t}{s}\right) \text{W} \quad p_{\max} := 150 \text{W}$$

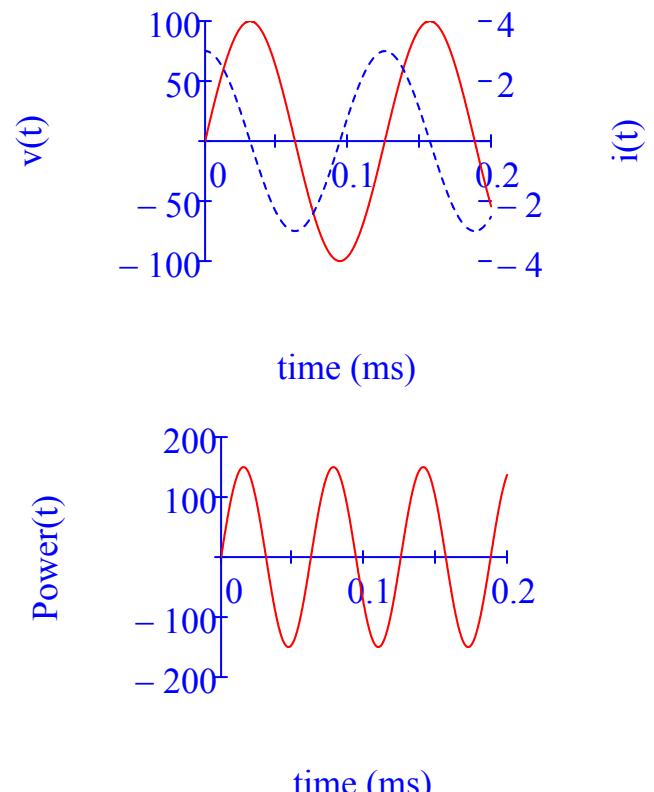c) $\text{energy}(t) := \int_0^t p(\tau) d\tau \quad \text{energy}\left(\frac{\pi}{100000} \text{s}\right) = 3 \cdot \text{mJ}$




The initial values of i_1 and i_2 in the circuit shown are + 3 A and - 5 A, respectively. The voltage at the terminals of the parallel inductors for $t > 0$ is

$$v(t) := -30e^{-50\frac{t}{s}} \text{ mV}$$

- a) If the parallel inductors are replaced by a single inductor, what is its inductance?
- b) What is the initial current and its reference direction in the equivalent inductor?
- c) Use the equivalent inductor to find $i(t)$.
- d) Find $i_1(t)$ and $i_2(t)$. Verify that the solutions for $i_1(t)$, $i_2(t)$, and $i(t)$ satisfy Kirchhoff's current law.

$$\frac{\text{mV} \cdot \text{s}}{\text{mH}} = 1 \text{ A}$$

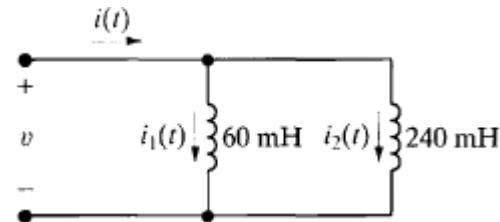d) $i_1(t) := \frac{1}{60} \cdot \frac{3}{5} e^{-50\frac{t}{s}} \text{ A} + 3 \text{ A}$ $i_2(t) := \frac{1}{240} \cdot \frac{3}{5} e^{-50\frac{t}{s}} \text{ A} - 5 \text{ A}$




a) $(60\text{mH}) \parallel (240\text{mH}) = 48 \cdot \text{mH}$

b) -2A Downward

c) $\int v(t) dt \rightarrow \frac{3 \cdot \text{mV} \cdot \text{s} \cdot e^{-50\frac{t}{s}}}{5}$

$i(t) := \frac{1}{48} \cdot \frac{3}{5} e^{-50\frac{t}{s}} \text{ A} + -2 \text{ A}$

$$i_1(t) + i_2(t) - i(t) \text{ simplify } \rightarrow 0$$

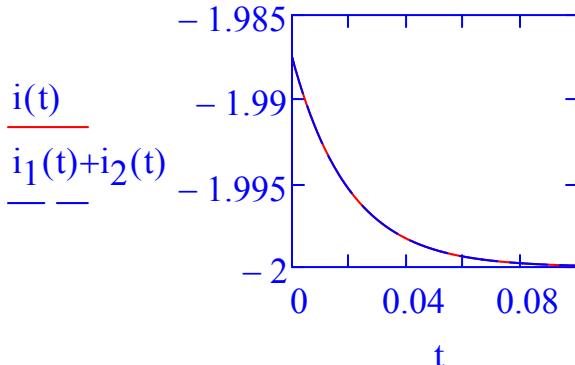

AP 6.5 The current at the terminals of the two capacitors shown is


$$i(t) := 240e^{-10\frac{t}{s}} \mu A \quad \text{for } t \geq 0$$

The initial values of v_1 and v_2 are -10V and -5V, respectively. Calculate the total energy trapped in the capacitors as $t \rightarrow \infty$ (Hint: Don't combine the capacitors in series—find the energy trapped in each, and then add.)

$$q_1 := 2\mu F \cdot -10V + q_{\text{inf}} = 4 \cdot \mu C$$

$$v_{1\text{inf}} := \frac{q_1}{2\mu F} = 2 V$$
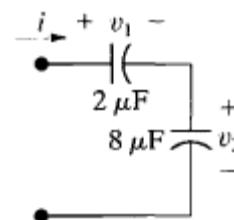
$$\text{energy}_1 := \frac{1}{2} \cdot 2\mu F \cdot v_{1\text{inf}}^2 = 4 \cdot \mu J$$



$$q_{\text{inf}} := \int_0^{\infty} i(t) dt = 24 \cdot \mu C$$

$$q_2 := 8\mu F \cdot -5V + q_{\text{inf}} = -16 \cdot \mu C$$

$$v_{2\text{inf}} := \frac{q_2}{8\mu F} = -2 V$$

$$\text{energy}_2 := \frac{1}{2} \cdot 8\mu F \cdot v_{2\text{inf}}^2 = 16 \cdot \mu J$$

$$\text{energy} := \text{energy}_1 + \text{energy}_2 = 20 \cdot \mu J$$

Note that the initial conditions for this problem are impractical as the two capacitors have unequal charges.

AP 6.6 a) Write a set of mesh-current equations for the circuit in Example 6.6. If the dot on the 4H inductor is at the right-hand terminal, the reference direction of i_g , is reversed, and the $60\ \Omega$ resistor is increased to $780\ \Omega$.
 b) Verify that if there is no energy stored in the circuit at $t = 0$, and if

$$i_g(t) := 1.96 \cdot \left(1 - e^{-\frac{4t}{s}} \right) A$$

the solutions to the differential equations derived in (a) of this Assessment Problem are

$$i_1(t) := \left(-0.4 - 11.6e^{-\frac{4t}{s}} + 12e^{-\frac{5t}{s}} \right) A$$

$$i_2(t) := \left(-0.01 - 0.99e^{-\frac{4t}{s}} + e^{-\frac{5t}{s}} \right) A$$


a)

$$4H \cdot \frac{d}{dt} i_1(t) - 8H \cdot \left[\frac{d}{dt} (-i_g(t) - i_2(t)) \right] + 20\Omega (i_1(t) - i_2(t)) + 5\Omega (i_1(t) + i_g(t)) = 0$$

$$20\Omega (i_2(t) - i_1(t)) + 780\Omega \cdot i_2(t) + 16H \cdot \frac{d}{dt} (i_2(t) + i_g(t)) + 8H \cdot \frac{d}{dt} i_1(t) = 0$$

rewriting :
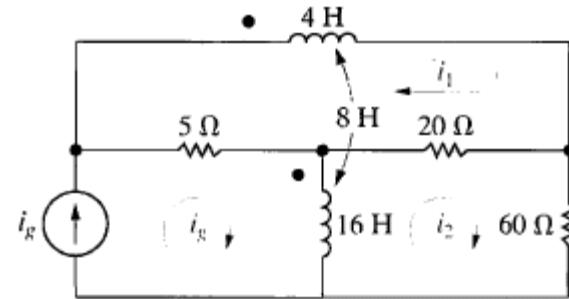
$$4 \cdot H \cdot \frac{d}{dt} i_1(t) + 25 \cdot \Omega \cdot i_1(t) + 8 \cdot H \cdot \frac{d}{dt} i_2(t) - 20\Omega \cdot i_2(t) = - \left(8 \cdot H \cdot \frac{d}{dt} i_g(t) + 5 \cdot \Omega \cdot i_g(t) \right)$$



$$8H \cdot \frac{d}{dt} i_1(t) - 20 \cdot \Omega \cdot i_1(t) + 16 \cdot H \cdot \frac{d}{dt} i_2(t) + 800 \cdot \Omega \cdot i_2(t) = -16 \cdot H \cdot \frac{d}{dt} i_g(t)$$

now check initial and final values.

$$i_1(0) = 0 \text{ A} \quad i_2(0) = 0 \text{ A}$$

$$i_1(\infty \cdot s) = -0.4 \text{ A} \quad i_2(\infty \cdot s) = -0.01 \text{ A}$$

$$i_{\text{final}} := i_g(\infty \cdot s) = 1.96 \text{ A} \quad v_{\text{final}} := (5 \parallel 20 \parallel 780)\Omega \cdot i_{\text{final}} = 7.8 \text{ V}$$

$$i_{1\text{final}} := \frac{-v_{\text{final}}}{(20 \parallel 780)\Omega} = -0.4 \text{ A} \quad i_{2\text{final}} := \frac{-v_{\text{final}}}{780\Omega} = -0.01 \text{ A}$$

$$t := 0$$

$$4 \cdot H \cdot \frac{d}{dt} i_1(t) + 25 \cdot \Omega \cdot i_1(t) + 8 \cdot H \cdot \frac{d}{dt} i_2(t) - 20 \Omega \cdot i_2(t) = - \left(8 \cdot H \cdot \frac{d}{dt} i_g(t) + 5 \cdot \Omega \cdot i_g(t) \right) \text{ simplify } \rightarrow 4.5438388140$$

$$4.5438388140730279993e-27 \cdot A \cdot \Omega = 0 \text{ V}$$

$$8H \cdot \frac{d}{dt} i_1(t) - 20 \cdot \Omega \cdot i_1(t) + 16 \cdot H \cdot \frac{d}{dt} i_2(t) + 800 \cdot \Omega \cdot i_2(t) = -16 \cdot H \cdot \frac{d}{dt} i_g(t) \text{ simplify } \rightarrow 1.6155871338926321775$$

$$1.6155871338926321775e-26 \cdot A \cdot \Omega = 0 \text{ V}$$