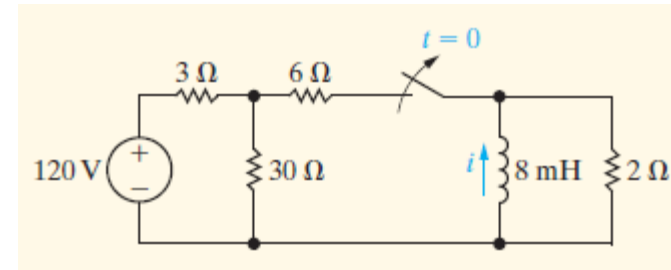


$$\|(a, b) := \frac{a \cdot b}{a + b}$$

AP 7.1 The switch in the circuit shown has been closed for a long time and is opened at $t = 0$.

- Calculate the initial value of i .
- Calculate the initial energy stored in the inductor.
- What is the time constant of the circuit for $t > 0$?
- What is the numerical expression for $i(t)$ for $t > 0$?
- What percentage of the initial energy stored has been dissipated in the 2Ω resistor 5 ms after the switch has been opened?




$$L := 8\text{mH} \quad R := 2\Omega$$

a) Thevenin eq. circuit for source has $V_{th} := \frac{30}{33} \cdot 120\text{V} = 109.091\text{V}$ $R_{th} := (30 \parallel 3 + 6)\Omega = 8.727\Omega$

so initial current is given by $i_0 := \frac{V_{th}}{R_{th}} = 12.5\text{A}$ b) $w_0 := \frac{1}{2} L \cdot i_0^2 = 625 \cdot \text{mJ}$

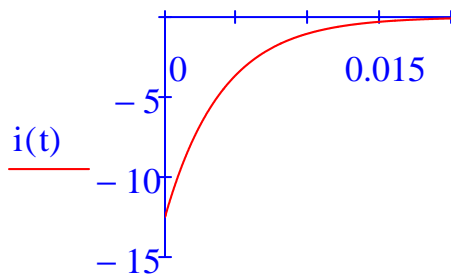c) $\tau := \frac{L}{R} = 4 \cdot \text{ms}$ d) $i(t) := -i_0 \cdot e^{-\frac{t}{\tau}}$ $i(t) \rightarrow -12.5 \cdot \text{A} \cdot e^{-\frac{250.0 \cdot t}{\text{s}}}$ $\text{mJ} \equiv 10^{-3}\text{J}$



$$w_5 := \frac{1}{2} L \cdot i(5\text{ms})^2 = 51.303 \cdot \text{mJ}$$


e) energy dissipated at 5ms:

$$1 - \frac{w_5}{w_0} = 91.8\%$$

AP 7.2 At $t = 0$, the switch in the circuit shown moves instantaneously from position a to position b.

a) Calculate v_o for $t > 0^+$.

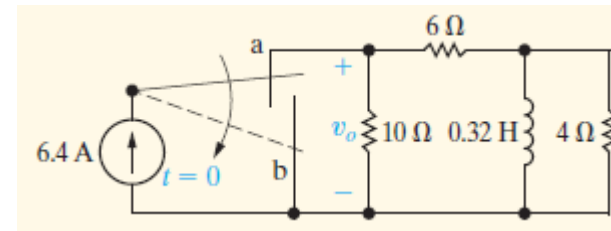b) What percentage of the initial energy stored in the inductor is eventually dissipated in the 4Ω , resistor?



a)

$$R := (16 \parallel 4)\Omega = 3.2 \Omega \quad L := 0.32\text{H} \quad \tau := \frac{L}{R} = 0.1 \text{ s}$$

$$i_0 := 6.4\text{A} \cdot \frac{(10 \parallel 6)}{6} = 4 \text{ A} \quad i_L(t) := i_0 \cdot e^{-\frac{t}{\tau}} \quad v_o(t) := -i_L(t) \cdot R \cdot \frac{10\Omega}{16\Omega}$$


$$\text{fix} := \frac{\text{V}}{\text{A} \cdot \Omega}$$

$$v_o(t) \rightarrow -8.0 \cdot \text{A} \cdot \Omega \cdot e^{-\frac{10.0 \cdot t}{\text{s}}} \quad \text{for } t \geq 0\text{s}$$

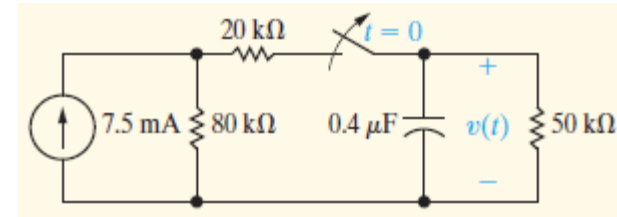b) $\frac{16\Omega}{16\Omega + 4\Omega} = 80\cdot\%$

AP 7.3 The switch in the circuit shown has been closed for a long time and is opened at $t = 0$. Find

- the initial value of $v(t)$,
- the time constant for $t > 0$,
- the numerical expression for $v(t)$ after the switch has been opened,
- the initial energy stored in the capacitor, and
- the length of time required to dissipate 75% of the initially stored energy.



$$R := 50\text{k}\Omega \quad C_1 := 0.4\mu\text{F}$$

$$\text{a) } v_0 := \frac{50}{70} \cdot (70 \parallel 80)\text{k}\Omega \cdot 7.5\text{mA} = 200 \text{ V}$$

$$\text{b) } \tau := R \cdot C_1 = 0.02 \text{ s}$$

$$\text{c) } v(t) := v_0 \cdot e^{-\frac{t}{\tau}} \quad v(t) \rightarrow 200 \cdot \text{V} \cdot e^{-\frac{50.0 \cdot t}{\text{s}}}$$


$$\text{d) } w_0 := \frac{1}{2} C_1 \cdot v_0^2 = 8 \cdot \text{mJ}$$

$$\text{e) } t_{75} := -\ln(\sqrt{25\%}) \cdot \tau = 13.86 \cdot \text{ms} \quad w_{75} := \frac{1}{2} \cdot C_1 \cdot v(t_{75})^2 = 2 \cdot \text{mJ}$$

AP 7.4 The switch in the circuit shown has been closed for a long time before being opened at $t = 0$.

a) Find $v_o(t)$ for $t > 0$.

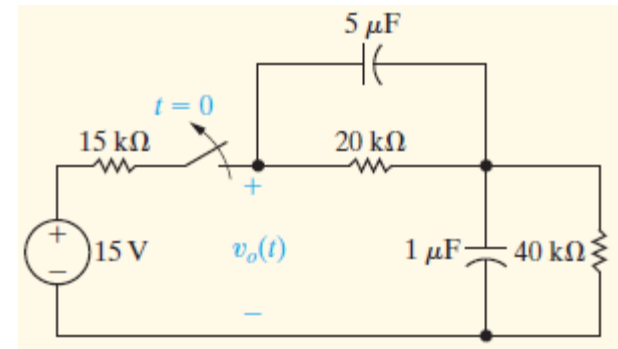b) What percentage of the initial energy stored in the circuit has been dissipated after the switch has been open for 60 ms?



a)

$$v_1 := \frac{20}{15 + 20 + 40} \cdot 15\text{V} = 4\text{V}$$

$$v_2 := \frac{40}{15 + 20 + 40} \cdot 15\text{V} = 8\text{V}$$

$$\tau_1 := 20\text{k}\Omega \cdot 5\mu\text{F} = 0.1\text{s}$$

$$\tau_2 := 40\text{k}\Omega \cdot 1\mu\text{F} = 0.04\text{s}$$

$$v(t) := v_1 \cdot e^{-\frac{t}{\tau_1}} + v_2 \cdot e^{-\frac{t}{\tau_2}}$$

$$v(t) \rightarrow 8 \cdot \text{V} \cdot e^{-\frac{25.0 \cdot t}{\text{s}}} + 4 \cdot \text{V} \cdot e^{-\frac{10.0 \cdot t}{\text{s}}}$$


b)

$$w_0 := \frac{1}{2} 5\mu\text{F} \cdot v_1^2 + \frac{1}{2} \cdot 1\mu\text{F} \cdot v_2^2 = 72 \cdot \mu\text{J}$$

$$w_{60} := \frac{1}{2} 5\mu\text{F} \cdot \left(v_1 \cdot e^{-\frac{60\text{ms}}{\tau_1}} \right)^2 + \frac{1}{2} \cdot 1\mu\text{F} \cdot \left(v_2 \cdot e^{-\frac{60\text{ms}}{\tau_2}} \right)^2$$


$$w_{60} = 13.641 \cdot \mu\text{J}$$
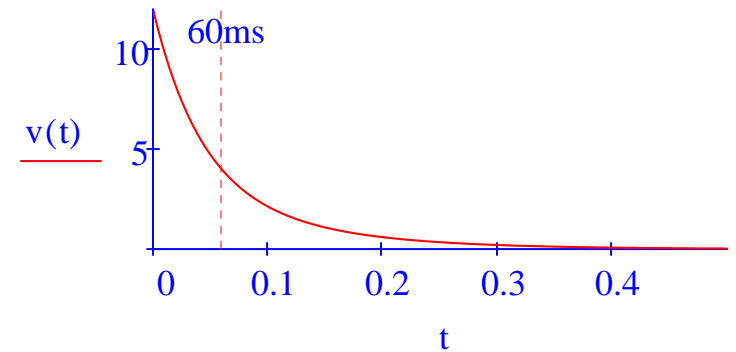
$$1 - \frac{w_{60}}{w_0} = 81.05 \cdot \%$$



$$\mu\text{J} \equiv 10^{-6}\text{J}$$

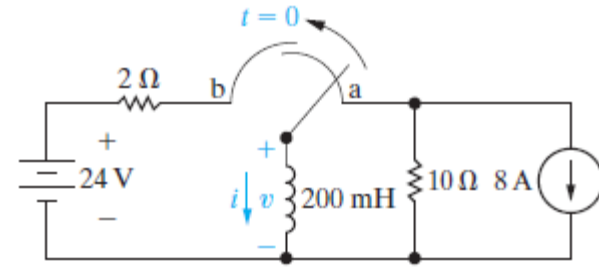AP 7.5 Assume that the switch in the circuit shown in Fig. 7.19 has been in position b for a long time, and at $t = 0$ it moves to position a. Find (a) $i(0^+)$; (b) $v(0^+)$; (c) τ , $t > 0$; (d) $i(t)$, $t > 0$; and (e) $v(t)$, $t > 0^+$.



a) $i_0 := \frac{24V}{2\Omega} = 12A$ $i_f := -8A$


b) $v_0 := -(i_0 + 8A) \cdot 10\Omega = -200V$

c) $\tau := \frac{200mH}{10\Omega} = 20 \cdot ms$ $\frac{1}{\tau} = 50 \frac{1}{s}$

d) $i(t) := (i_0 - i_f)e^{\frac{-t}{\tau}} + i_f$ $i(t) := \left(20e^{\frac{-50t}{s}} - 8\right) \cdot A$

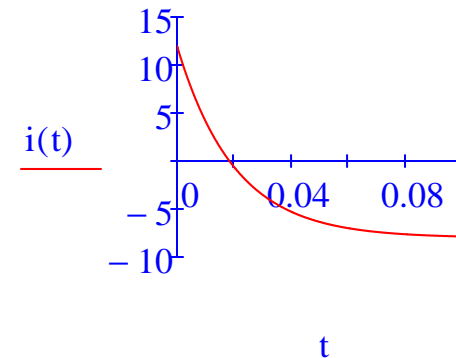
e) $v(t) := 200mH \left(\frac{d}{dt} i(t) \right)$

$$v(t) \rightarrow -\frac{200000 \cdot A \cdot mH \cdot e^{-\frac{50 \cdot t}{s}}}{s} = -200e^{-\frac{50t}{s}} V$$



$$\frac{A \cdot mH}{s} = 1 \times 10^{-3} V$$

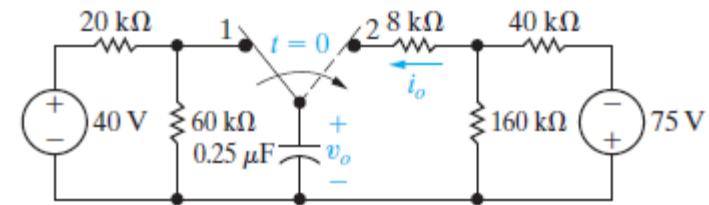- AP 7.6 a) Find the expression for the voltage across the 160 kΩ resistor in the circuit shown in Fig. 7.22. Let this voltage be denoted v_A , and assume that the reference polarity for the voltage is positive at the upper terminal of the 160 kΩ resistor.
- b) Specify the interval of time for which the expression obtained in (a) is valid.



a)

$$v_{A0} := -75V \cdot \frac{160}{200} = -60V$$

$$v_{o0} := 40V \cdot \frac{60}{80} = 30V$$

using superposition, short out the 75V supply, leaving

$$R := (8 + 40 \parallel 160)k\Omega = 40 \cdot k\Omega \quad \text{so} \quad \tau := R \cdot 0.25\mu F = 0.01s$$


$$v_o(t) := (v_{o0} - v_{A0})e^{-\frac{t}{\tau}} + v_{A0} \quad v_o(t) \rightarrow 90 \cdot V \cdot e^{-\frac{100.0 \cdot t}{s}} - 60 \cdot V$$

$$v_A(t) := (v_{o0} - v_{A0}) \cdot e^{-\frac{t}{\tau}} \cdot \frac{(160 \parallel 40)}{(160 \parallel 40) + 8} + v_{A0}$$

$$v_A(t) \rightarrow 72 \cdot V \cdot e^{-\frac{100.0 \cdot t}{s}} - 60 \cdot V$$

b) for $t > 0$


AP 7.7

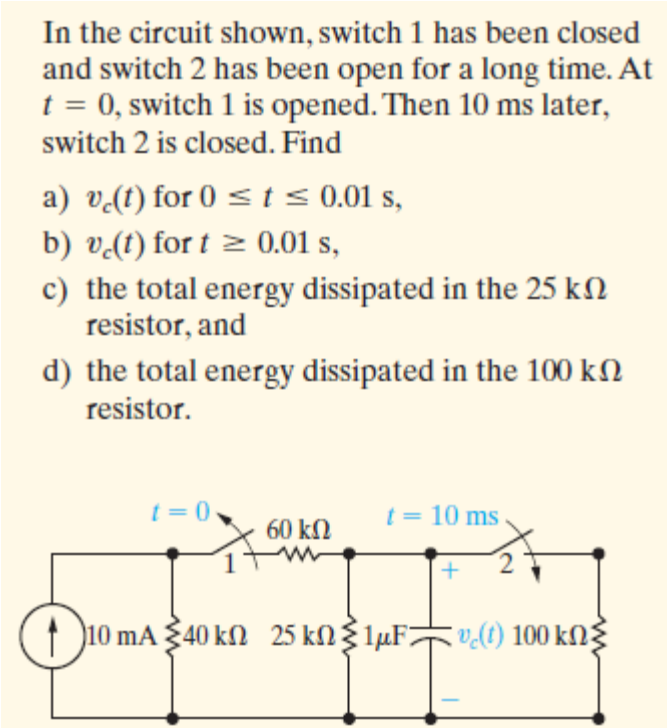

$$v_{c0} := \frac{25}{25 + 60 + 40} \cdot 10\text{mA} \cdot 40\text{k}\Omega = 80 \text{ V}$$

$$\frac{1}{25\text{k}\Omega \cdot 1\mu\text{F}} = 40 \frac{1}{\text{s}} \qquad \frac{1}{(25 \parallel 100)\text{k}\Omega \cdot 1\mu\text{F}} = 50 \frac{1}{\text{s}}$$
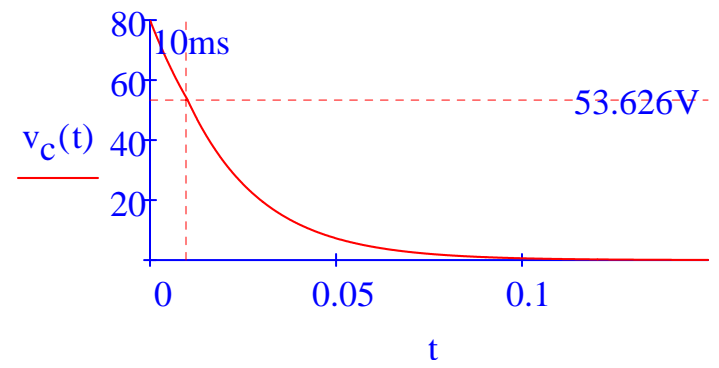
$$v_c(t) := \begin{cases} v_{c0} & \text{if } t < 0 \\ v_{c0} \cdot e^{\frac{-40t}{\text{s}}} & \text{if } 0 \leq t \leq 10\text{ms} \\ 53.626e^{\frac{-50(t-10\text{ms})}{\text{s}}} \text{ V} & \text{otherwise} \end{cases}$$



$$w_0 := \frac{1}{2} \cdot \mu\text{F} \cdot v_{c0}^2 = 3.2 \cdot \text{mJ}$$

$$w_{10} := \frac{1}{2} \mu\text{F} \cdot v_c(10\text{ms})^2 = 1.438 \cdot \text{mJ}$$

$$\text{c) } w_{25} := (w_0 - w_{10}) + \left(\frac{100}{125}\right) \cdot w_{10} = 2.912 \cdot \text{mJ}$$

$$\text{d) } w_{100} := \frac{25}{125} \cdot w_{10} = 0.288 \cdot \text{mJ}$$


$$w_{25} + w_{100} = 3.2 \cdot \text{mJ}$$

$$\int_{0\text{s}}^{200\text{ms}} \frac{v_c(t)^2}{25\text{k}\Omega} dt = 2.912 \cdot \text{mJ}$$

$$\int_{10\text{ms}}^{200\text{ms}} \frac{v_c(t)^2}{100\text{k}\Omega} dt = 0.288 \cdot \text{mJ}$$

AP 7.8

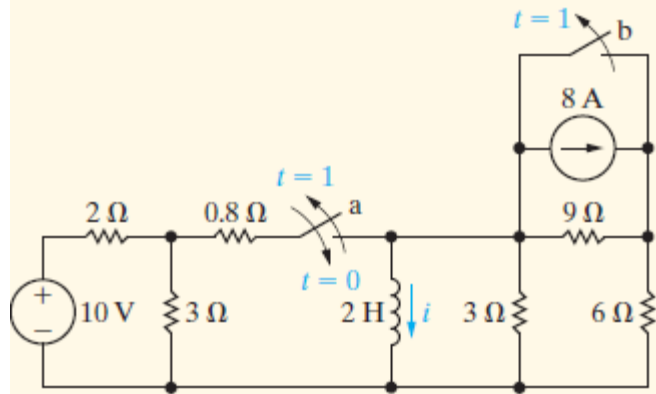Switch a in the circuit shown has been open for a long time, and switch b has been closed for a long time. Switch a is closed at $t = 0$ and, after remaining closed for 1 s, is opened again. Switch b is opened simultaneously, and both switches remain open indefinitely. Determine the expression for the inductor current i that is valid when (a) $0 \leq t \leq 1$ s and (b) $t \geq 1$ s.



a)
$$i_1(t) := \left(3 - 3e^{\frac{-0.5t}{s}} \right) \text{A}$$

$$i_{2s} - i_{2f} = 5.98 \text{ A}$$

b)
$$i_2(t) := \left[-4.8 + 5.98 \cdot e^{\frac{-1.25(t-1s)}{s}} \right] \text{A}$$

$$6 \parallel 3 = 2 \quad 3 \parallel 2 + 0.8 = 2$$

$$\tau_1 := \frac{2\text{H}}{1\Omega} = 2\text{ s} \quad \frac{1}{\tau_1} = 0.5 \frac{1}{\text{s}}$$

$$V_{\text{Th}} := \frac{3}{3+2} \cdot 10\text{V} = 6\text{ V} \quad i_{f1} := \frac{V_{\text{Th}}}{2\Omega} = 3\text{ A}$$


$$i_{2s} := \left(1 - e^{\frac{-1}{2}} \right) \cdot i_{f1} = 1.18\text{ A}$$

$$V_{\text{Th}} := 8\text{A} \cdot 9\Omega = 72\text{ V}$$

$$R_{\text{Th}} := (9 + 6)\Omega = 15\Omega \quad i_{2f} := \frac{-V_{\text{Th}}}{R_{\text{Th}}} = -4.8\text{ A}$$

$$\tau_2 := \frac{2\text{H}}{R_{\text{Th}} \parallel (3\Omega)} = 0.8\text{ s} \quad \frac{1}{\tau_2} = 1.25 \frac{1}{\text{s}}$$

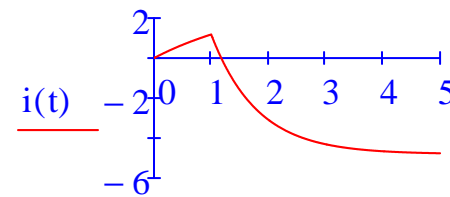
$$i(t) := \begin{cases} i_{f1} \cdot \left(1 - e^{\frac{-0.5 \cdot t}{s}} \right) & \text{if } 0 \leq t \leq 1\text{ s} \\ \left[i_{2f} + (i_{2s} - i_{2f}) \cdot e^{\frac{-1.25(t-1s)}{s}} \right] & \text{if } t > 1\text{ s} \end{cases}$$



t

AP 7.9

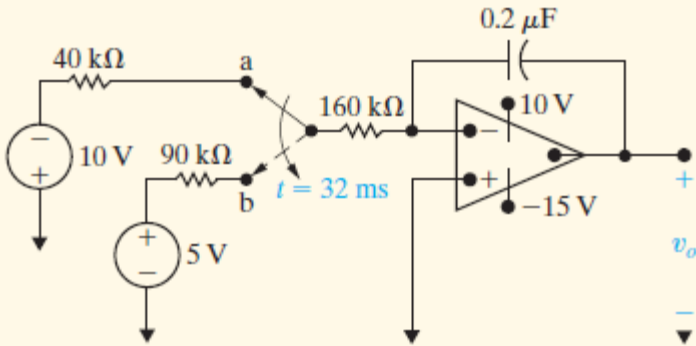7.9 There is no energy stored in the capacitor at the time the switch in the circuit makes contact with terminal a. The switch remains at position a for 32 ms and then moves instantaneously to position b. How many milliseconds after making contact with terminal a does the op amp saturate?



$$i_1 := \frac{-10\text{V}}{(40 + 160)\text{k}\Omega} = -50 \cdot \mu\text{A}$$

$$v_{32} := \frac{32\text{ms} \cdot -i_1}{0.2\mu\text{F}} = 8\text{V}$$


$$i_2 := \frac{5\text{V}}{(90 + 160)\text{k}\Omega} = 20 \cdot \mu\text{A} \quad \Delta t := \text{ms}$$

Given $i_2 \cdot \Delta t = (8\text{V} + 15\text{V}) \cdot 0.2\mu\text{F}$ Find(Δt) = 230 · ms

$$t := 32\text{ms} + 230\text{ms} = 262 \cdot \text{ms}$$

AP 7.10

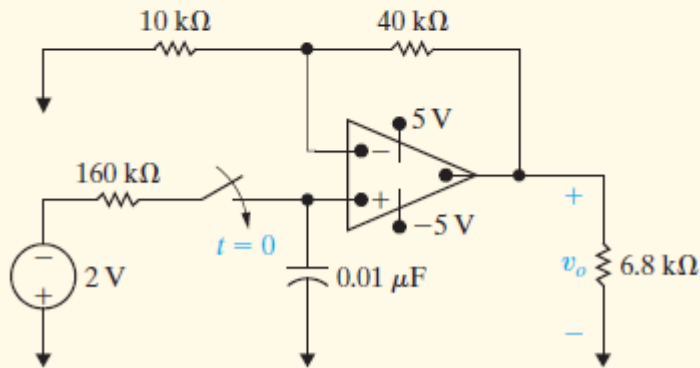- 7.10 a) When the switch closes in the circuit shown, there is no energy stored in the capacitor. How long does it take to saturate the op amp?
 b) Repeat (a) with an initial voltage on the capacitor of 1 V, positive at the upper terminal.



non-inverting configuration implies gain of 5

so saturation will occur when input voltage hits -1V

$$\tau := 160\text{k}\Omega \cdot 0.01\mu\text{F} = 1.6 \cdot \text{ms}$$

$$i_{\text{in}}(t) := \frac{-2\text{V}}{160\text{k}\Omega} \cdot e^{\frac{-t}{1.6\text{ms}}}$$

voltage is decaying to half of eventual so

$$\text{a) } -\ln(.5) \cdot \tau = 1.109 \cdot \text{ms}$$

$$\text{verify: } \frac{1}{0.01\mu\text{F}} \cdot \int_0^{1.109\text{ms}} i_{\text{in}}(t) dt = -1\text{V}$$

voltage is decaying to 1/3 of eventual so

$$\text{b) } -\ln\left(\frac{1}{3}\right) \cdot \tau = 1.758 \cdot \text{ms}$$

$$i_{\text{inb}}(t) := \frac{-3\text{V}}{160\text{k}\Omega} \cdot e^{\frac{-t}{\tau}}$$

$$\text{verify: } \frac{1}{0.01\mu\text{F}} \cdot \int_0^{1.758\text{ms}} i_{\text{inb}}(t) dt + 1\text{V} = -1\text{V}$$