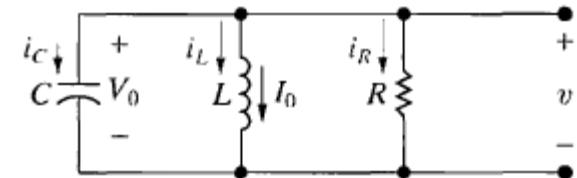


Mathcad Solutions to Assessment Problems from Nilsson and Riedel  
*Electric Circuits* 9th edition, © 2012 R. Doering.  
 Chapter 8

AP 8.1 The resistance and inductance of the circuit in Fig. 8.5 are  $100 \Omega$  and  $20 \text{ mH}$ , respectively.

- Find the value of  $C$  that makes the voltage response critically damped.
- If  $C$  is adjusted to give a neper frequency of  $5 \text{ krad/s}$ , find the value of  $C$  and the roots of the characteristic equation.
- If  $C$  is adjusted to give a resonant frequency of  $20 \text{ krad/s}$ , find the value of  $C$  and the roots of the characteristic equation.



useful functions:

$$\alpha(RC) := \frac{1}{2RC} \quad \text{neper frequency}$$

$$\omega_0(LC) := \frac{1}{\sqrt{LC}} \quad \text{radian resonant frequency}$$

characteristic roots:

$$s_1(R, L, C) := -\alpha(R \cdot C) + \sqrt{\alpha(R \cdot C)^2 - \omega_0(L \cdot C)^2}$$

$$s_2(R, L, C) := -\alpha(R \cdot C) - \sqrt{\alpha(R \cdot C)^2 - \omega_0(L \cdot C)^2}$$

$$\text{overdamped}(R, L, C) := \omega_0(L \cdot C)^2 < \alpha(R \cdot C)^2$$

$$\text{underdamped}(R, L, C) := \omega_0(L \cdot C)^2 > \alpha(R \cdot C)^2$$

$$\text{criticallydamped}(R, L, C) := \omega_0(L \cdot C)^2 = \alpha(R \cdot C)^2$$

$$R := 100\Omega \quad L := 20\text{mH}$$

$$\text{krad} \equiv 10^3 \text{rad}$$

a) Given criticallydamped( $R, L, C_1$ ) = 1     $C_1 := \text{Find}(C_1) \rightarrow \frac{mH}{2000 \cdot \Omega^2}$      $C_1 = 0.5 \cdot \mu F$

b) Given  $\alpha(R \cdot C_2) = 5 \frac{krad}{s}$      $C_2 := \text{Find}(C_2) \rightarrow \frac{s}{1000000 \cdot \Omega \cdot rad}$      $C_2 = 1 \cdot \mu F$

$$s_1(R, L, C_2) = (-5 + 5j) \cdot \frac{krad}{s} \quad s_2(R, L, C_2) = (-5 - 5j) \cdot \frac{krad}{s}$$

c) Given  $\omega_0(L \cdot C_3) = 20 \frac{krad}{s}$      $C_3 := \text{Find}(C_3) \rightarrow \frac{s^2}{8000000000 \cdot mH \cdot rad^2}$      $C_3 = 0.125 \cdot \mu F$

$$s_1(R, L, C_3) = -5.359 \cdot \frac{krad}{s} \quad s_2(R, L, C_3) = -74.641 \cdot \frac{krad}{s}$$

```

rlc(R1,L1,C1,v0,dv0dt) := | if criticallydamped(R1,L1,C1)
| | | D2 ← v0
| | | αc ← α(R1·C1)
| | | D1 ← dv0dt + αc·D2
| | | return ( 3 - D1·s / V - D2 / V αc·s - 1 )T
| | s1 ← s1(R1,L1,C1)
| | s2 ← s2(R1,L1,C1)
| | A ← ( 1 1 )-1 · ( v0 )
| | | s1·s s2·s ( dv0dt·s )
| | return ( 1 A0 / V A1 / V s1·s s2·s )T if overdamped(R1,L1,C1)
| otherwise
| | B ← [ A0 + A1 ]
| | | j · ( A0 - A1 )
| | ωd ← s1 - s2 / 2j
| | α ← s1 + s2 / -2
| | | ( 2 B0 B1 )T

```

|    | return (  $\angle$   $\frac{V}{V}$   $\frac{\alpha \cdot s}{V}$   $\omega_d \cdot s$  )

$$v_{rlc}(A, t) := V \cdot \begin{cases} A_1 e^{A_3 \frac{t}{s}} + A_2 e^{A_4 \cdot \frac{t}{s}} & \text{if } A_0 = 1 \\ \left( A_1 \cdot \cos\left(A_4 \cdot \frac{t}{s}\right) + A_2 \cdot \sin\left(A_4 \cdot \frac{t}{s}\right) \right) \cdot e^{-A_3 \frac{t}{s}} & \text{if } A_0 = 2 \\ \left( A_1 \frac{t}{s} + A_2 \right) \cdot e^{-A_3 \frac{t}{s}} & \text{if } A_0 = 3 \\ 0 & \text{otherwise} \end{cases}$$

$C_1 := \text{undef}$        $C_1 := C_1$

```

simpRlc(R1,L1,C1,v0,i0,I) := 
  | iL0 <- i0
  | vC0 <- v0
  | f <- 1 / (2π · √(L1 · C1))
  | NN <- 2048 · 8 - 2
  | Δt <- 2^(floor(log(4 / (f · NN · s), 2)))
  | for n ∈ 0 .. NN
    |   | vCn+1 <- vCn + (I - iLn - vCn / R1) · Δt / C1
    |   | iLn+1 <- iLn + vCn+1 · Δt / L1
  | return (augment(vC / V, iL / A), Δt / s)

```

Ex 8.2

$$\text{S} := \text{rlc}\left(200\Omega, 50\text{mH}, 0.2\mu\text{F}, 12\text{V}, -450 \frac{\text{kV}}{\text{s}}\right)$$

$$\text{S}^T = \begin{pmatrix} 1 & -14 & 26 & -5 \times 10^3 & -2 \times 10^4 \end{pmatrix}$$


$$\text{S} := \begin{pmatrix} 1 & -14 & 26 & -5 \times 10^3 & -2 \times 10^4 \end{pmatrix}^T$$

$$v(t) := v_{\text{rlc}}(\text{S}, t)$$

$$v(t) \rightarrow -V \cdot \begin{pmatrix} -\frac{5000 \cdot t}{\text{s}} & -\frac{20000 \cdot t}{\text{s}} \\ 14 \cdot e^{-\frac{5000 \cdot t}{\text{s}}} & -26 \cdot e^{-\frac{20000 \cdot t}{\text{s}}} \end{pmatrix}$$

$$v(t) := \begin{pmatrix} -5000 \frac{t}{\text{s}} & -20000 \frac{t}{\text{s}} \\ -14e^{-\frac{5000 \cdot t}{\text{s}}} + 26e^{-\frac{20000 \cdot t}{\text{s}}} \end{pmatrix} V$$

$$v(t) := v_{\text{rlc}}(\text{S}, t)$$

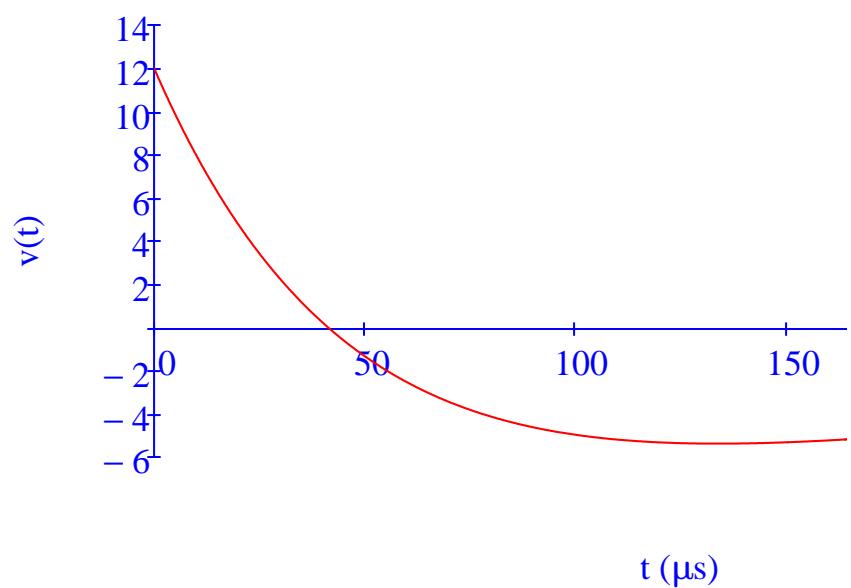


$r1 := 200\Omega$

$\begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(r1, 50mH, 0.2\mu F, 12V, 30mA, 0A)$

$\text{rows}(X) = 16384$

$n := 0..16383$

Simulation

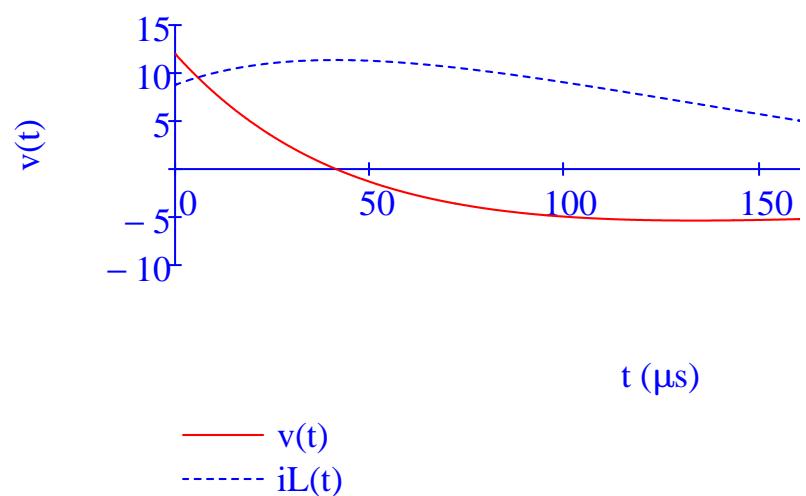


AP 8.2

Use the integral relationship between  $i_L$  and  $v$  to find the expression for  $i_L$  in Fig. 8.6.


r:  $i_L(t) = (56e^{-5000t} - 26e^{-20,000t}) \text{ mA}, t \geq 0.$
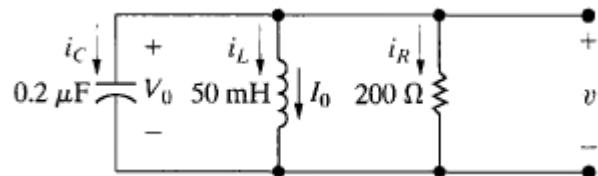
$$i_L(t) := \frac{1}{50\text{mH}} \cdot \int_0^t v(u) \, du + 30 \frac{\text{V}\cdot\text{s}}{\text{mH}} \cdot 10^{-6}$$




$$i_L(t) \cdot \frac{\text{mH}}{\text{V}\cdot\text{s}} \cdot \frac{\text{mA}}{10^{-6}} \text{ expand } \rightarrow 56 \cdot \text{mA} \cdot e^{-\frac{5000 \cdot t}{\text{s}}} - 26 \cdot \text{mA} \cdot e^{-\frac{20000 \cdot t}{\text{s}}}$$
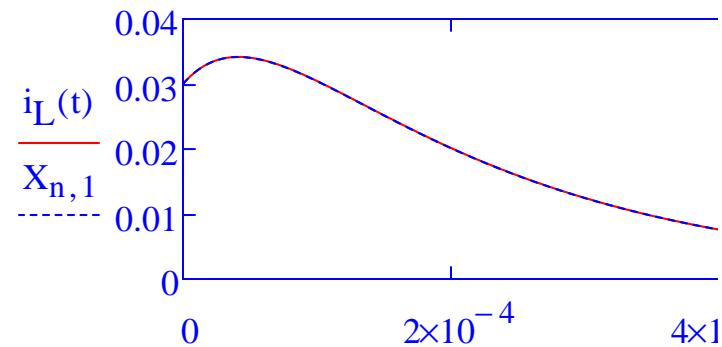
$$\frac{\text{mH}}{\text{V}\cdot\text{s}} \cdot \frac{\text{mA}}{10^{-6}} = 1$$



AP 8.3 The element values in the circuit shown are  $R = 2 \text{ k}\Omega$ ,  $L = 250 \text{ mH}$ , and  $C = 10 \text{ nF}$ . The initial current  $I_0$  in the inductor is  $-4 \text{ A}$ , and the initial voltage on the capacitor is  $0 \text{ V}$ . The output signal is the voltage  $v$ . Find (a)  $i_R(0^+)$ ; (b)  $i_C(0^+)$ ; (c)  $dv(0^+)/dt$ ; (d)  $A_1$ ; (e)  $A_2$ ; and (f)  $v(t)$  when  $t > 0$ .

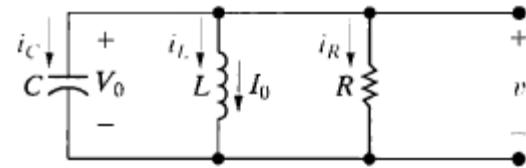

$$R_3 := 2\text{k}\Omega \quad L_3 := 250\text{mH} \quad C_3 := 10\text{nF}$$

a)  $i_R(0) := 0\text{A}$

b)  $i_C(0) := 4\text{A}$       c)  $dv/dt := \frac{4\text{A}}{C_3} = 4 \times 10^8 \cdot \frac{\text{V}}{\text{s}}$

d)  $S := \text{rlc}(R_3, L_3, C_3, 0\text{V}, dv/dt)$        $A1 := S_1 = 13333$

e)  $A2 := S_2 = -13333$        $S^T = (1 \ 13333 \ -13333 \ -10000 \ -40000)$



$$S := (1 \ 13333 \ -13333 \ -10000 \ -40000)^T$$

f)  $v_3(t) := v_{\text{rlc}}(S, t)$

$$v_3(t) \rightarrow V \cdot \left( 13333 \cdot e^{-\frac{10000 \cdot t}{s}} - 13333 \cdot e^{-\frac{40000 \cdot t}{s}} \right)$$

$$v(t) := 13333 \cdot \left( e^{-10000 \frac{t}{s}} - e^{-40000 \frac{t}{s}} \right) V$$

$$\begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(R_3, L_3, C_3, 0V, -4A, 0A)$$

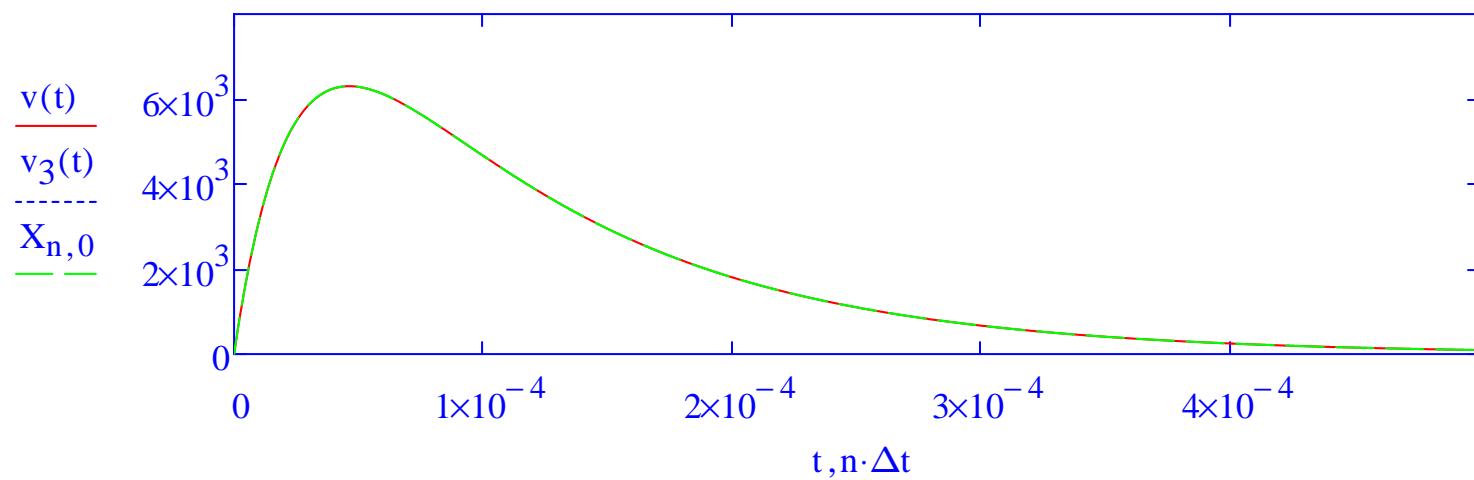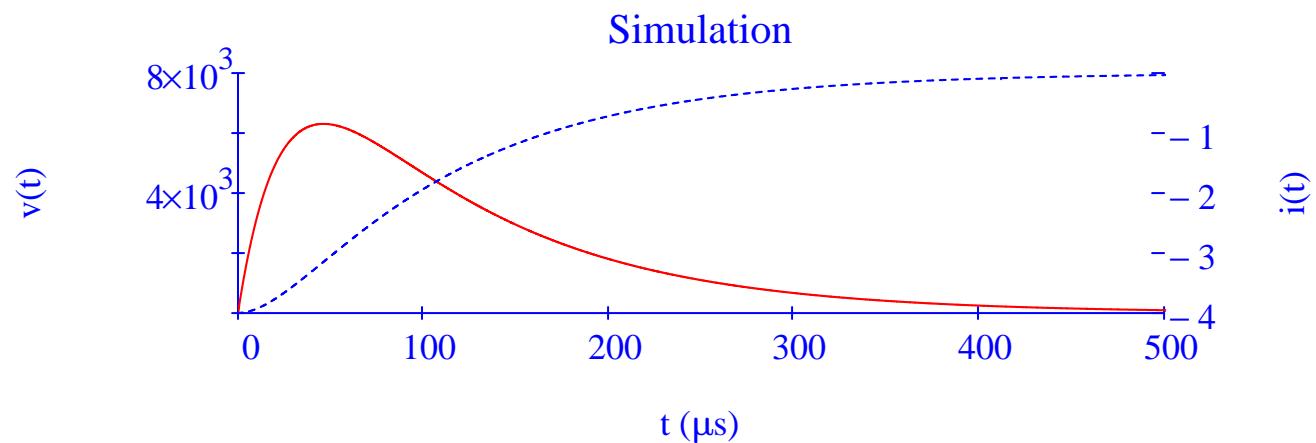

Ex 8.4

$$R_4 := 20k\Omega \quad L_4 := 8H \quad C_4 := 0.125\mu F$$


$$S := \text{rlc}\left(R_4, L_4, C_4, 0V, 98000 \frac{V}{s}\right)$$

$$S^T = (2 \ 0 \ 100.021 \ 200 \ 979.796) \quad S := (2 \ 0 \ 100.021 \ 200 \ 979.796)^T$$

$$v(t) := v_{\text{rlc}}(S, t)$$

$$v(t) \rightarrow 100.021 \cdot V \cdot \sin\left(\frac{979.796 \cdot t}{s}\right) \cdot e^{-\frac{200 \cdot t}{s}}$$
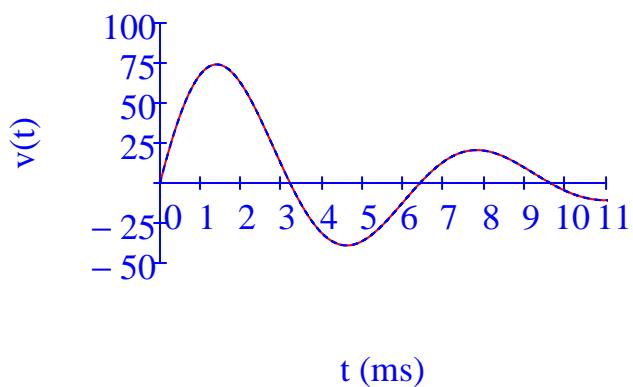
$$\begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(R_4, L_4, C_4, 0V, -12.25mA, 0A)$$



$$\alpha_4 := \alpha(R_4 \cdot C_4) = 200 \frac{1}{s}$$

$$\omega_d(R, L, C) := \sqrt{\omega_0(L \cdot C)^2 - \alpha(R \cdot C)^2}$$

$$a) \quad s_1(R_4, L_4, C_4) = (-200 + 979.796j) \frac{1}{s}$$


$$s_2(R_4, L_4, C_4) = (-200 - 979.796j) \frac{1}{s}$$

$$\omega_4 := \omega_d(R_4, L_4, C_4) = 979.796 \frac{1}{s}$$

$$b) \quad dv/dt := \frac{12.25mA}{C_4} = 9.8 \times 10^4 \cdot \frac{V}{s}$$


$$c) \quad B_2 := \frac{dv/dt}{\omega_4} = 100.021 V$$
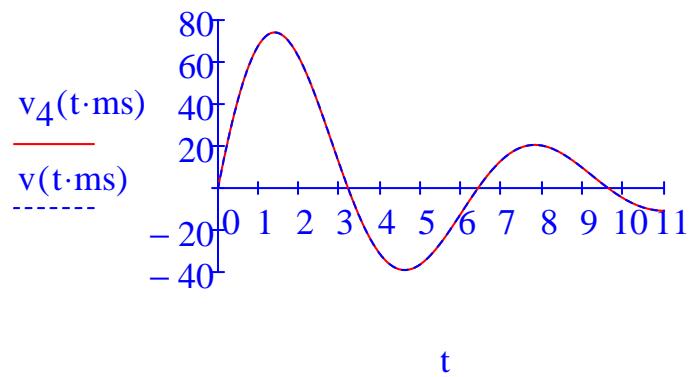
$$d) \quad v_4(t) := B_2 \cdot e^{-\alpha_4 \cdot \frac{t}{s}} \cdot \sin\left(\omega_4 \cdot \frac{t}{s}\right) V$$



AP 8.4 A 10 mH inductor, a 1  $\mu$ F capacitor, and a variable resistor are connected in parallel in the circuit shown. The resistor is adjusted so that the roots of the characteristic equation are  $-8000 \pm j6000$  rad/s. The initial voltage on the capacitor is 10 V, and the initial current in the inductor is 80 mA. Find

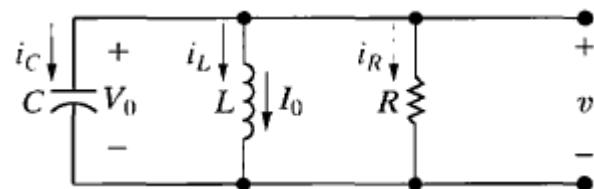- a) R;
- b)  $dv(0^+)/dt$ ;
- c)  $B_1$  and  $B_2$  in the solution for v; and
- d)  $i_L(t)$ .



$$L_{84} := 10\text{mH} \quad C_{84} := 1\mu\text{F}$$

a) Given  $s_1(R_x, L_{84}, C_{84}) = (-8000 + j \cdot 6000) \frac{\text{rad}}{\text{s}}$   $R_{84} := \text{Find}(R_x) \rightarrow \frac{(80000 - 60000j) \cdot \text{mH}}{s^2 - [(-960000000 - 280000000j)]}$

$$R_{84} = 62.5 \Omega$$

$$s_1(R_{84}, L_{84}, C_{84}) = (-8 + 6j) \cdot \frac{\text{krad}}{\text{s}} \quad s_2(R_{84}, L_{84}, C_{84}) = (-8 - 6j) \cdot \frac{\text{krad}}{\text{s}}$$


$$\text{b) } \frac{dv}{dt} := \frac{-80\text{mA} - \frac{10\text{V}}{R_{84}}}{C_{84}} = -0.24 \cdot \frac{\text{V}}{\mu\text{s}}$$

$$\text{c) } B := \text{rlc}(R_{84}, L_{84}, C_{84}, 10\text{V}, \frac{dv}{dt}) \quad B_1 = 10 \quad B_2 = -26.667$$

$$B^T = \begin{pmatrix} 2 & 10 & -26.667 & 8 \times 10^3 & 6 \times 10^3 \end{pmatrix}$$

$$d) \quad v(t) := 10V \cdot e^{-8000 \cdot \frac{t}{s}} \cdot \cos\left(6000 \cdot \frac{t}{s}\right) - 26 \frac{2}{3} V \cdot e^{-8000 \cdot \frac{t}{s}} \cdot \sin\left(6000 \cdot \frac{t}{s}\right)$$
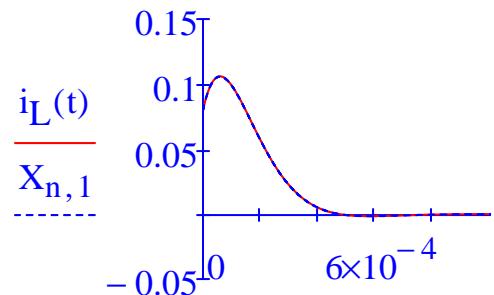
$$i_L(t) := \frac{1}{L_{84}} \cdot \int_0^t v(u) du + 80mA \quad \begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(R_{84}, L_{84}, C_{84}, 10V, 80mA, 0A)$$



$t, n \cdot \Delta t$

Ex 8.5

$$L_5 := 0.4\text{H} \quad C_5 := 10\mu\text{F}$$

$$\text{mJ} \equiv 10^{-3}\text{J}$$

Given     criticallydamped( $R_4, L_4, C_4$ ) = 1

$$R_5 := \text{Find}(R_4) \rightarrow \begin{pmatrix} -\frac{4.0 \cdot H^{0.5}}{\mu F^{0.5}} & \frac{4.0 \cdot H^{0.5}}{\mu F^{0.5}} \end{pmatrix} \quad R_5 = (-4000 \ 4000) \Omega$$

$$R_4 := 4000\Omega$$


$$v_0 := 0\text{V} \quad dvdt := 98000 \frac{\text{V}}{\text{s}}$$

$$\alpha_{cd} := \alpha(R_4 \cdot C_4) = 1 \times 10^3 \frac{1}{\text{s}}$$

$$D := \text{rlc}(R_4, L_4, C_4, v_0, dvdt) \quad D^T = (3 \ 98000 \ 0 \ 1000 \ 1)$$

$$D_2 := v_0 \quad D_1 := dvdt + \alpha_{cd} \cdot D_2 \quad D_1 = 98000 \cdot \frac{\text{V}}{\text{s}} \quad D_2 = 0$$
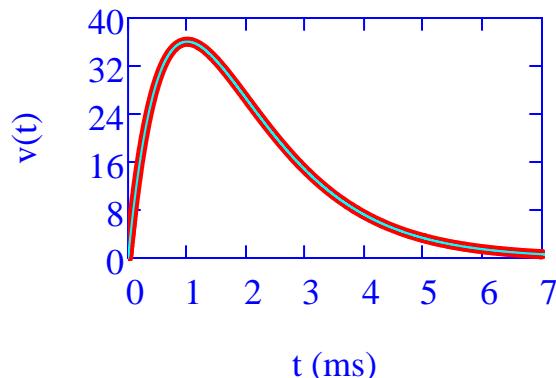
$$v(t) := D_1 \cdot t \cdot e^{-\alpha_{cd} \cdot t} + D_2 \cdot e^{-\alpha_{cd} \cdot t} \quad \begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(R_4, L_4, C_4, v_0, -12.25\text{mA}, 0\text{A})$$





## AP 8.5 The resistor in the circuit in Assessment

Problem 8.4 is adjusted for critical damping.

The inductance and capacitance values are 0.4 H and 10  $\mu$ F, respectively. The initial energy stored in the circuit is 25 mJ and is distributed equally between the inductor and capacitor.

Find (a) R; (b)  $V_0$ ; (c)  $I_0$ ; (d)  $D_1$  and  $D_2$  in the solution for v; and (e)  $i_R$ ,  $t > 0$ .

$$L_5 := 0.4\text{H} \quad C_5 := 10\mu\text{F}$$

Given    criticallydamped( $R_x, L_5, C_5$ ) = 1     $R_5 := \text{Find}(R_x) \rightarrow \left( -\frac{0.1 \cdot H^{0.5}}{\mu F^{0.5}} \quad \frac{0.1 \cdot H^{0.5}}{\mu F^{0.5}} \right)$

$$R_5 = (-100 \quad 100)\Omega \quad R_5 := 100\Omega$$

$$v_0 := \sqrt{\frac{25\text{mJ}}{C_5}} = 50\text{V} \quad i_{L0} := \sqrt{\frac{25\text{mJ}}{L_5}} = 250\cdot\text{mA} \quad dvdt := \frac{-i_{L0} - \frac{v_0}{R_5}}{C_5} = -7.5 \times 10^4 \cdot \frac{\text{V}}{\text{s}}$$

$$D := \text{rlc}(R_5, L_5, C_5, v_0, dvdt) \quad D_1 = -50000 \quad D_2 = 50 \quad D_3 = 500$$


$$D^T = (3 \quad -5 \times 10^4 \quad 50 \quad 500 \quad 1) \quad D := (3 \quad -5 \times 10^4 \quad 50 \quad 500 \quad 1)^T$$

$$v(t) := v_{rlc}(D, t)$$

$$\begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(R_5, L_5, C_5, v_0, 250\text{mA}, 0\text{A})$$


$$v(t) \rightarrow -V \cdot e^{-\frac{500 \cdot t}{s}} \cdot \left( \frac{50000 \cdot t}{s} - 50 \right)$$
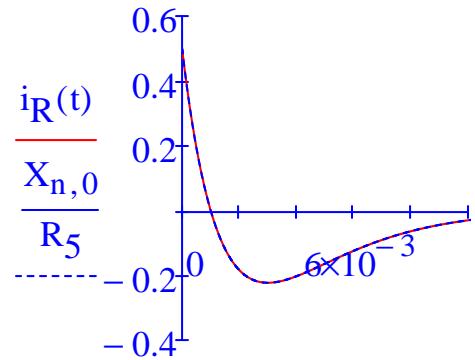
$$i_R(t) := \frac{v(t)}{R_5} \cdot \frac{A \cdot \Omega}{V} \text{ expand} \rightarrow \frac{A \cdot e^{-\frac{500 \cdot t}{s}}}{2} - \frac{500 \cdot A \cdot t \cdot e^{-\frac{500 \cdot t}{s}}}{s}$$



$t, n \cdot \Delta t$

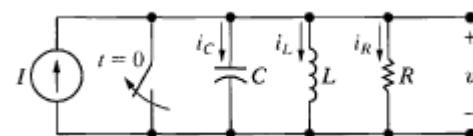AP 8.6 In the circuit shown,  $R = 500 \Omega$ ,  $L = 0.64 \text{ H}$ ,  $C = 1 \mu\text{F}$ , and  $I = -1 \text{ A}$ . The initial voltage drop across the capacitor is  $40 \text{ V}$  and the initial inductor current is  $0.5 \text{ A}$ . Find (a)  $i_R(0^+)$ ; (b)  $i_C(0^+)$ ; (c)  $di_L(0^+)/dt$ ; (d)  $s_1, s_2$ ; (e)  $i_L(t)$  for  $t > 0$ ; and (f)  $v(t)$  for  $t > 0+$ .



$$R_6 := 500\Omega \quad L_6 := 0.64\text{H} \quad C_6 := 1\mu\text{F} \quad I := -1\text{A} \quad v_{c0} := 40\text{V} \quad i_{L0} := 0.5\text{A}$$

$$\begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simprlc}(R_6, L_6, C_6, v_{c0}, i_{L0}, I)$$

$$\text{a)} \quad i_{R0} := \frac{v_{c0}}{R_6} = 80 \cdot \text{mA}$$

$$\text{b)} \quad i_{c0} := I - i_{L0} - i_{R0} = -1.58 \text{ A}$$

$$\text{c)} \quad di_{L0}/dt := \frac{v_{c0}}{L_6} = 62.5 \frac{\text{A}}{\text{s}}$$

$$\text{d)} \quad s_1(R_6, L_6, C_6) = (-1000 + 750j) \cdot \frac{\text{rad}}{\text{s}} \quad s_2(R_6, L_6, C_6) = (-1000 - 750j) \cdot \frac{\text{rad}}{\text{s}}$$

$$\text{e)} \quad B := \text{rlc}\left(R_6, L_6, C_6, v_{c0}, \frac{I - i_{L0} - \frac{v_{c0}}{R_6}}{C_6}\right)$$

$$B^T = (2 \ 40 \ -2053.33 \ 1000 \ 750)$$

$$B := (2 \ 40 \ -2053.33 \ 1000 \ 750)^T$$


$$v(t) := v_{\text{rlc}}(B, t)$$

$$f) \quad v(t) \rightarrow V \cdot e^{-\frac{1000 \cdot t}{s}} \cdot \left( 40 \cdot \cos\left(\frac{750 \cdot t}{s}\right) + -2053.33 \cdot \sin\left(\frac{750 \cdot t}{s}\right) \right)$$


$$B1 := -I + i_{L0} = 1.5 \text{ A}$$

$$62.5 \text{ A} = 750 B2 - 1000 \cdot B1 \text{ solve, } B2 \rightarrow 2.0 \cdot A + 0.08333333333333333 \cdot A$$
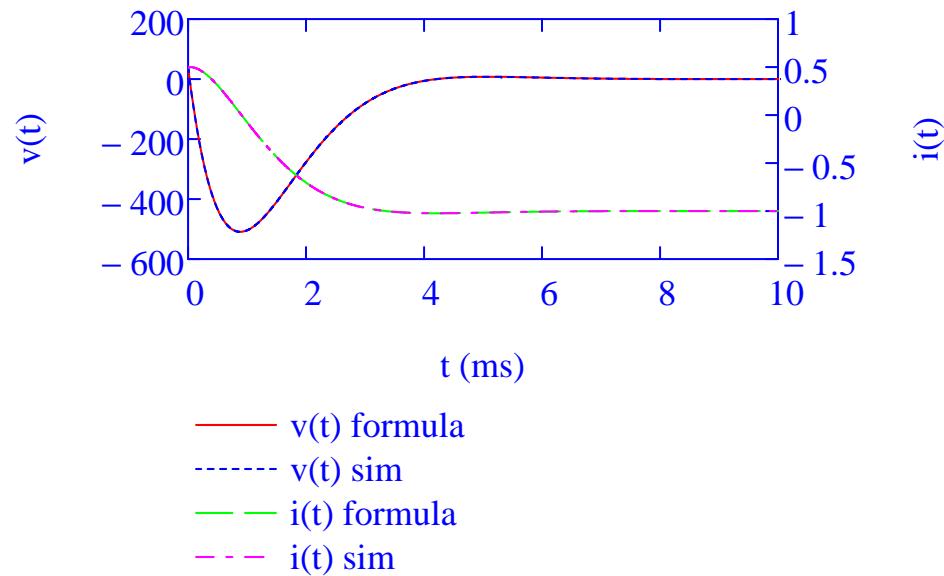
$$i(t) := I + e^{-\frac{1000 \cdot t}{s}} \cdot \left( 1.5 \cos\left(750 \frac{t}{s}\right) + 2.0833 \cdot \sin\left(750 \cdot \frac{t}{s}\right) \right) \cdot A$$



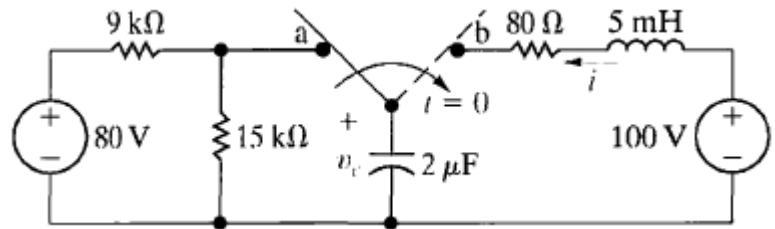AP 8.7 The switch in the circuit shown has been in position a for a long time. At  $t = 0$ , it moves to position b. Find (a)  $i(0^+)$ ; (b)  $v_c(0^+)$ ; (c)  $di(0^+)/dt$ ; (d)  $s_1, s_2$ ; and (e)  $i(t)$  for  $t > 0$ .



```

simsrlc(R1,L1,C1,vc0,iL0,vf) := 
    iL0 ← iL0
    vc0 ← vc0
    f ← 1 / (2π · √(L1 · C1))
    NN ← 2048 · 8 - 2
    Δt ← 2^(floor(log(4 / (f · NN · s), 2)))
    for n ∈ 0 .. NN
        vc_{n+1} ← vc_n + iL_n · Δt / C1
        iL_{n+1} ← iL_n + (vf - iL_n · R1 - vc_n) · Δt / L1
    return augment(vc / V, iL / A)
    Δt / s
  
```

$$R_7 := 80\Omega \quad L_7 := 5\text{mH} \quad C_7 := 2\mu\text{F} \quad v_f := 100\text{V}$$

$$\text{a)} \quad i(O) := 0\text{A} \quad \text{b)} \quad v_{c0} := \frac{15}{9+15} \cdot 80\text{V} = 50\text{V} \quad \text{c)} \quad \text{didt} := \frac{v_f - v_{c0}}{L_7} = 10000 \frac{\text{A}}{\text{s}}$$

$$R := R \quad L := L$$

$$s^2 + \frac{R}{L}s + \frac{1}{L \cdot C} = 0 \text{ solve, } s \rightarrow \left[ \begin{array}{l} -\frac{R - \sqrt{-\frac{1}{C} \cdot (4 \cdot L - C \cdot R^2)}}{2 \cdot L} \\ -\frac{R + \sqrt{-\frac{4 \cdot L - C \cdot R^2}{C}}}{2 \cdot L} \end{array} \right]$$

$$\text{roots}(R, L, C) := \left[ \begin{array}{l} 0 \\ -\frac{R - \sqrt{-\frac{1}{C} \cdot (4 \cdot L - C \cdot R^2)}}{2 \cdot L} \\ -\frac{R + \sqrt{-\frac{4 \cdot L - C \cdot R^2}{C}}}{2 \cdot L} \end{array} \right]$$

$$\text{d)} \quad S := \text{roots}(R_7, L_7, C_7) \quad S_1 = (-8000 + 6000j) \cdot \frac{\text{rad}}{\text{s}} \quad S_2 = (-8000 - 6000j) \cdot \frac{\text{rad}}{\text{s}}$$

$$\alpha_s(R, L) := \frac{R}{2L} \quad \alpha_7 := \alpha_s(R_7, L_7) = 8000 \cdot \frac{\text{rad}}{\text{s}} \quad \omega_7 := 6000 \frac{\text{rad}}{\text{s}}$$

$$B_1 := i(0) = 0 \quad e^{-\alpha_7 \cdot t} \cdot (B_2 \cdot \sin(\omega_7 \cdot t)) \quad B_2 := B_2$$


$$B_2 \cdot \omega_7 \cdot e^{-t \cdot \alpha_7} \cdot \cos(t \cdot \omega_7) - B_2 \cdot \alpha_7 \cdot e^{-t \cdot \alpha_7} \cdot \sin(t \cdot \omega_7) \text{ assume, } t = 0\text{s} \rightarrow \frac{6000 \cdot B_2 \cdot \text{rad}}{\text{s}}$$

$$\frac{6000 \cdot B_2 \cdot \text{rad}}{\text{s}} = 10000 \frac{\text{A}}{\text{s}} \text{ solve, } B_2 \rightarrow \frac{5 \cdot \text{A}}{3 \cdot \text{rad}} \quad B_2 := \frac{5}{3} \text{A} = 1.667 \text{ A}$$

$$i(t) := e^{-\alpha_7 \cdot t} \cdot (B_1 \cdot \cos(\omega_7 \cdot t) + B_2 \cdot \sin(\omega_7 \cdot t))$$

$$i(t) \rightarrow 1.666666666666667 \cdot A \cdot e^{-\frac{8000 \cdot t}{s}} \cdot \sin\left(\frac{6000 \cdot \text{rad} \cdot t}{s}\right)$$
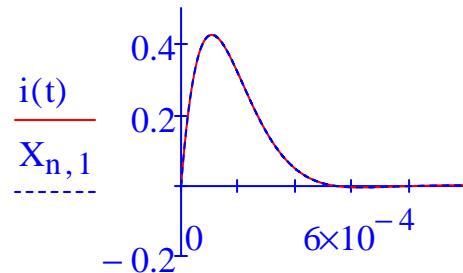
$$\begin{pmatrix} X \\ \Delta t \end{pmatrix} := \text{simsrlc}(R_7, L_7, C_7, v_{c0}, 0A, 100V)$$



$t, n \cdot \Delta t$

AP 8.8 Find  $v_c(t)$  for  $t > 0$  for the circuit in  
Assessment Problem 8.7.

$$B_1 := 50V \quad B_2 := B_2$$

$$e^{-\alpha_7 \cdot t} \cdot (B_1 \cdot \cos(\omega_7 \cdot t) + B_2 \cdot \sin(\omega_7 \cdot t))$$

$$e^{-t \cdot \alpha_7} \cdot (B_2 \cdot \omega_7 \cdot \cos(t \cdot \omega_7) - B_1 \cdot \omega_7 \cdot \sin(t \cdot \omega_7)) - \alpha_7 \cdot e^{-t \cdot \alpha_7} \cdot (B_1 \cdot \cos(t \cdot \omega_7) + B_2 \cdot \sin(t \cdot \omega_7))$$

$$B_2 \cdot \omega_7 - B_1 \cdot \alpha_7 = 0 \frac{V}{s} \text{ solve for } B_2 \rightarrow \frac{200 \cdot V \cdot s}{3 \cdot s \cdot \text{rad}} \quad B_2 := \frac{200}{3} V$$

$$v_c(t) := v_f - e^{-\alpha_7 \cdot t} \cdot (B_1 \cdot \cos(\omega_7 \cdot t) + B_2 \cdot \sin(\omega_7 \cdot t))$$

$$v_c(t) \rightarrow 100 \cdot V - e^{-\frac{8000 \cdot t}{s}} \cdot \left( 50 \cdot V \cdot \cos\left(\frac{6000 \cdot \text{rad} \cdot t}{s}\right) + \frac{200 \cdot V \cdot \sin\left(\frac{6000 \cdot \text{rad} \cdot t}{s}\right)}{3} \right)$$

